

[illegible]

Resistor

Switch


Wire

Battery

Cell


Light Bulb





## Electric Charge

Charles-Augustin de Coulomb  
1736-1806

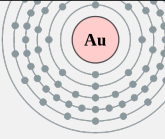

- The charge of a single electron is  $1.6021 \times 10^{-19}$  Coulombs
- or... it would take  $6.241 \times 10^{18}$  electrons to have a Coulomb of charge
- 1 Ampere is a current of that many electrons every second.

6


---

---

---

---

---

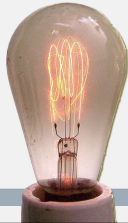

## Electric Power

# P = I V

$P = V^2/R$   
 $P = I^2 R$   
 Power (Watt)

7

---


---

---

---

---

## Resistors in Series



- The Charges have to “fight” through every resistor. This decreases the total current.

Voltage:  $V_T = V_1 + V_2 + V_3$   
 Current:  $I_T = I_1 = I_2 = I_3$   
 Resistance:  $R_T = R_1 + R_2 + R_3$

8

---


---

---

---

---

## Resistors in Series



The current starts at the top of the battery and follows a single path, clockwise, around the circuit.

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>			2	
R <sub>2</sub>			4	
R <sub>3</sub>			6	
TOTAL	24			

9

---


---

---

---

---

## Resistors in Series



Start with the total resistance, a simple sum of the individual values

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>			2	
R <sub>2</sub>			4	
R <sub>3</sub>			6	
TOTAL	24		12	

10

---

---

---

---

---

### Resistors in Series

In a series circuit, there is only one current, so that value can be applied to each resistor.

	V (V)	I (A)	R ( $\Omega$ )	P (W)
R <sub>1</sub>		2	2	
R <sub>2</sub>		2	4	
R <sub>3</sub>		2	6	
TOTAL	24	2	12	

12

---

---

---

---

---

---

---

---

### Resistors in Series

When you have two values for a resistor, equations will get you the other numbers.  
 $V = I R$   
 $V_1 = 2 \times 2 = 4 \text{ Volts}$

	V (V)	I (A)	R ( $\Omega$ )	P (W)
R <sub>1</sub>	4	2	2	
R <sub>2</sub>	8	2	4	
R <sub>3</sub>	12	2	6	
TOTAL	24	2	12	

13

---

---

---

---

---

---

---

---

### Resistors in Parallel

- The Charges have a choice of paths to follow.
- This decreases the total resistance.

Voltage:  $V_T = V_1 = V_2 = V_3$   
 Current:  $I_T = I_1 + I_2 + I_3$   
 Resistance:  $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$

15

---

---

---

---

---

---

---

---

### Resistors in Parallel

	V (V)	I (A)	R ( $\Omega$ )	P (W)
R <sub>1</sub>			120	
R <sub>2</sub>			60	
R <sub>3</sub>			10	
TOTAL	12			

16

---

---

---

---

---

---

---

---

### Resistors in Parallel

Add the resistors inversely.  
 $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$   
 $1/R_T = 1/120 + 1/60 + 1/10$   
 $R_T = 8 \Omega$

	V (V)	I (A)	R ( $\Omega$ )	P (W)
R <sub>1</sub>			120	
R <sub>2</sub>			60	
R <sub>3</sub>			10	
TOTAL	12		8 $\Omega$	

17

---

---

---

---

---

---

---

---

### Resistors in Parallel

If you are given the total Voltage (EMF), resistors in parallel all have the same Voltage.

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>	12		120	
R <sub>2</sub>	12		60	
R <sub>3</sub>	12		10	
TOTAL	12		8 Ω	

18

---

---

---

---

---

---

### Resistors in Parallel

Use Ohm's Law to find the currents  
 $V = I R$   
 $12 = I_1 \times 120$   
 $I_1 = 0.1 \text{ Amperes}$

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>	12	0.1	120	
R <sub>2</sub>	12	0.2	60	
R <sub>3</sub>	12	1.2	10	
TOTAL	12	1.5	8 Ω	

19

---

---

---

---

---

---

### Resistors in Combination Circuits

- Some of the resistors are in Series, some are in Parallel
- Find simple groups that are only one or the other
- Find an Equivalent Resistance for that section
- Keep combining the sections until the circuit is simple

21

---

---

---

---

---

---

### Resistors in Combination

This one starts with the parallel component.  
 Make another resistor that will replace R<sub>2</sub> and R<sub>3</sub>.

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>			4	
R <sub>2</sub>			18	
R <sub>3</sub>			9	
TOTAL	60			

22

---

---

---

---

---

---

### Resistors in Combination

A parallel combination of 18 and 9 can be replaced by a 6 ohm resistor.  
 With that equivalent resistor replacing R<sub>2</sub> and R<sub>3</sub> the circuit looks like a simple series circuit.

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>			4	
R <sub>2</sub>			18	
R <sub>3</sub>			9	
TOTAL	60			

23

---

---

---


---

---

---



### Resistors in Combination

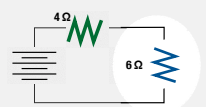

The new series of 6 and 4 creates a total resistance of 10 ohms.

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>			4	
R <sub>2</sub>			18	
R <sub>3</sub>			9	
TOTAL	60		10	

24

---

---

---

---


---

---

---

---

### Resistors in Combination

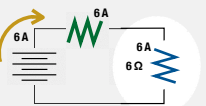

Use Ohm's Law to find a total current of 6 amperes.  
This is the current throughout each series section.

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>		6	4	
R <sub>2</sub>			18	
R <sub>3</sub>			9	
TOTAL	60	6	10	

25

---

---

---

---


---

---

---

---

### Resistors in Combination

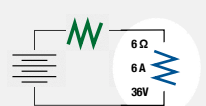

Solve for 3 values of the replacement resistor.  
V, I, and R

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>		6	4	
R <sub>2</sub>			18	
R <sub>3</sub>			9	
TOTAL	60	6	10	

26

---

---

---

---


---

---

---

---

### Resistors in Combination

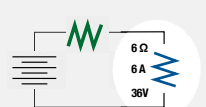

Uncover the original circuit, keep the voltage for parallel components.  
(if the original is a series, keep the current)

	V (V)	I (A)	R (Ω)	P (W)
R <sub>1</sub>	24	6	4	
R <sub>2</sub>	36		18	
R <sub>3</sub>	36		9	
TOTAL	60	6	10	

27

---

---

---


---

---

---

---

---

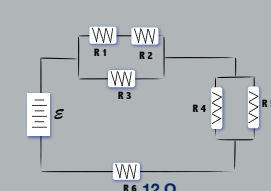

### Practice

	V	I	R	P
1			10	
2			6	
3			30	
4			40	
5			10	
6			12	
T	180			

30

---

---

---

---

---

---

---


---

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9

32

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9



Green, Blue, Brown, Gold

5                      6                      0 (1)

**560 Ω ± 5%**

33

Black 0  
Brown 1  
Red 2  
Orange 3  
Yellow 4  
Green 5  
Blue 6  
Violet 7  
Gray 8  
White 9

Brown, Black, Orange, Gold  
1 0 000 (3)  
 $10,000 \Omega \pm 5\%$   
10 k $\Omega$

34

# Resistance

$$R = \frac{\rho L}{A}$$

- Resistance  $\Omega$
- resistivity  $\Omega\text{m}$
- length  $\text{m}$
- area  $\text{m}^2$


Material	Resistivity $\rho$ ( $\Omega\text{-m}$ )	Material	Resistivity $\rho$ ( $\Omega\text{-m}$ )
<b>Insulators</b>		<b>Semiconductors</b>	
Aluminum	$2.82 \times 10^{-8}$	Carbon	$3.5 \times 10^4$
Copper	$1.72 \times 10^{-8}$	Germanium	$60^{\circ}\text{C}$
Gold	$2.44 \times 10^{-8}$	Silicon	$200\text{--}2300^{\circ}\text{C}$
Iron	$9.7 \times 10^{-8}$	<b>Insulators</b>	
Mercury	$95.8 \times 10^{-8}$	Mica	$10^9\text{--}10^{11}$
Nichrome (alloy)	$100 \times 10^{-8}$	Rubber (hard)	$10^9\text{--}10^{14}$
Silver	$1.29 \times 10^{-7}$	Teflon	$10^{10}$
Tungsten	$5.6 \times 10^{-8}$	Wood (moist)	$3 \times 10^8$

The values given for semiconductors are at  $20^{\circ}\text{C}$ .

Resistivity  $\rho$

35

## You Have 5 Resistors



6Ω      12Ω      12Ω      36Ω      36Ω

36

36

### Biggest Possible Total?

102  $\Omega$

6 $\Omega$  12 $\Omega$  12 $\Omega$  36 $\Omega$  36 $\Omega$

37

---

---

---

---

---

### How could you get...

60  $\Omega$

6 $\Omega$  12 $\Omega$  12 $\Omega$  36 $\Omega$  36 $\Omega$

39

---

---

---

---

---

### Kirchhoff's Rules

Gustav Robert Kirchhoff  
1824-1887

43

---

---

---

---

---

**The Point Rule-**  
The sum of current going in to a point must equal the sum of current coming out.

$$\Sigma I_{in} = \Sigma I_{out}$$

$$\Sigma I = 0$$

44

---

---

---

---

---

**The Loop Rule-**  
A closed path that begins and ends at the same point will have no net change in potential.

$$\Sigma V = 0$$

45


---

---

---

---

---

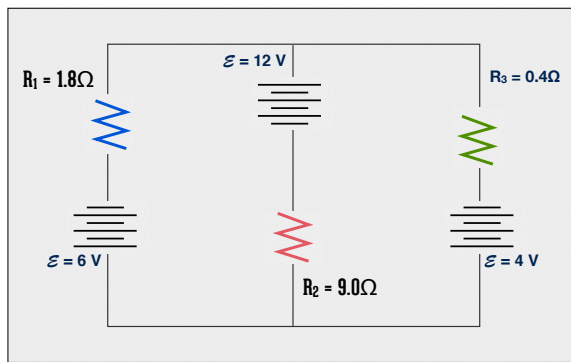

46

---


---

---

---

---

---

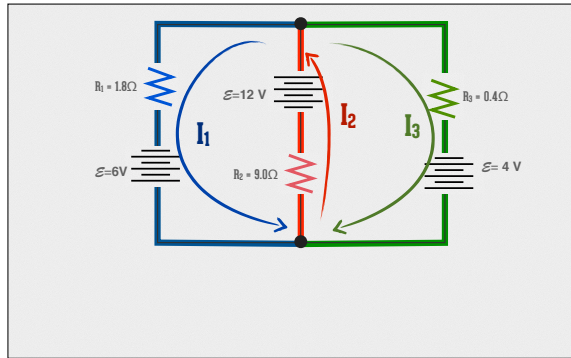

47

---


---

---

---

---

---

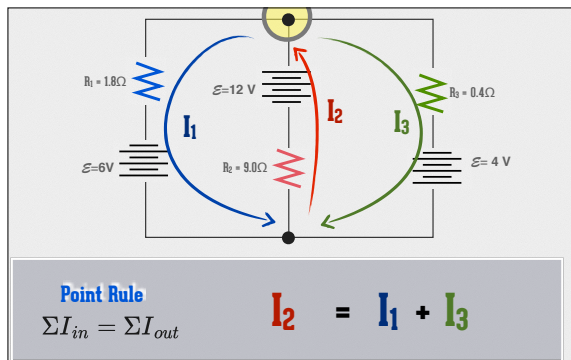

48

---


---

---

---

---

---

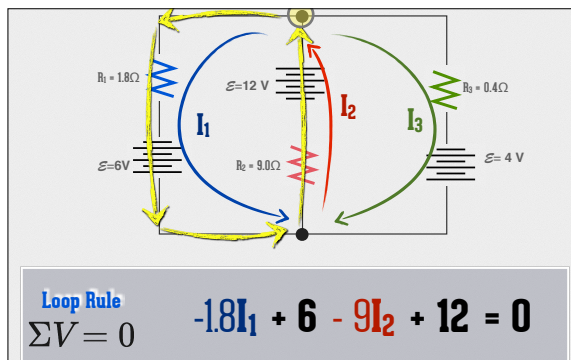

49

---


---

---

---

---

---

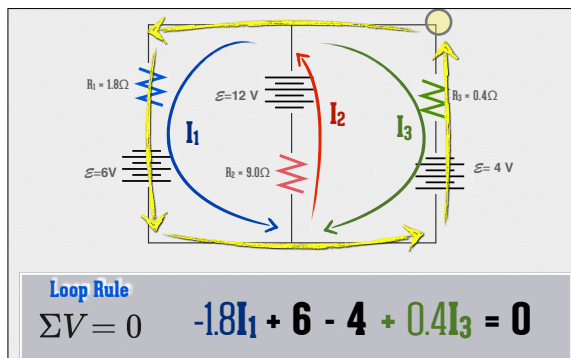

50

---

---

---

---

---

---