

Capacitors




What is inside a flashlight?

Battery?


Bulb?

Switch?



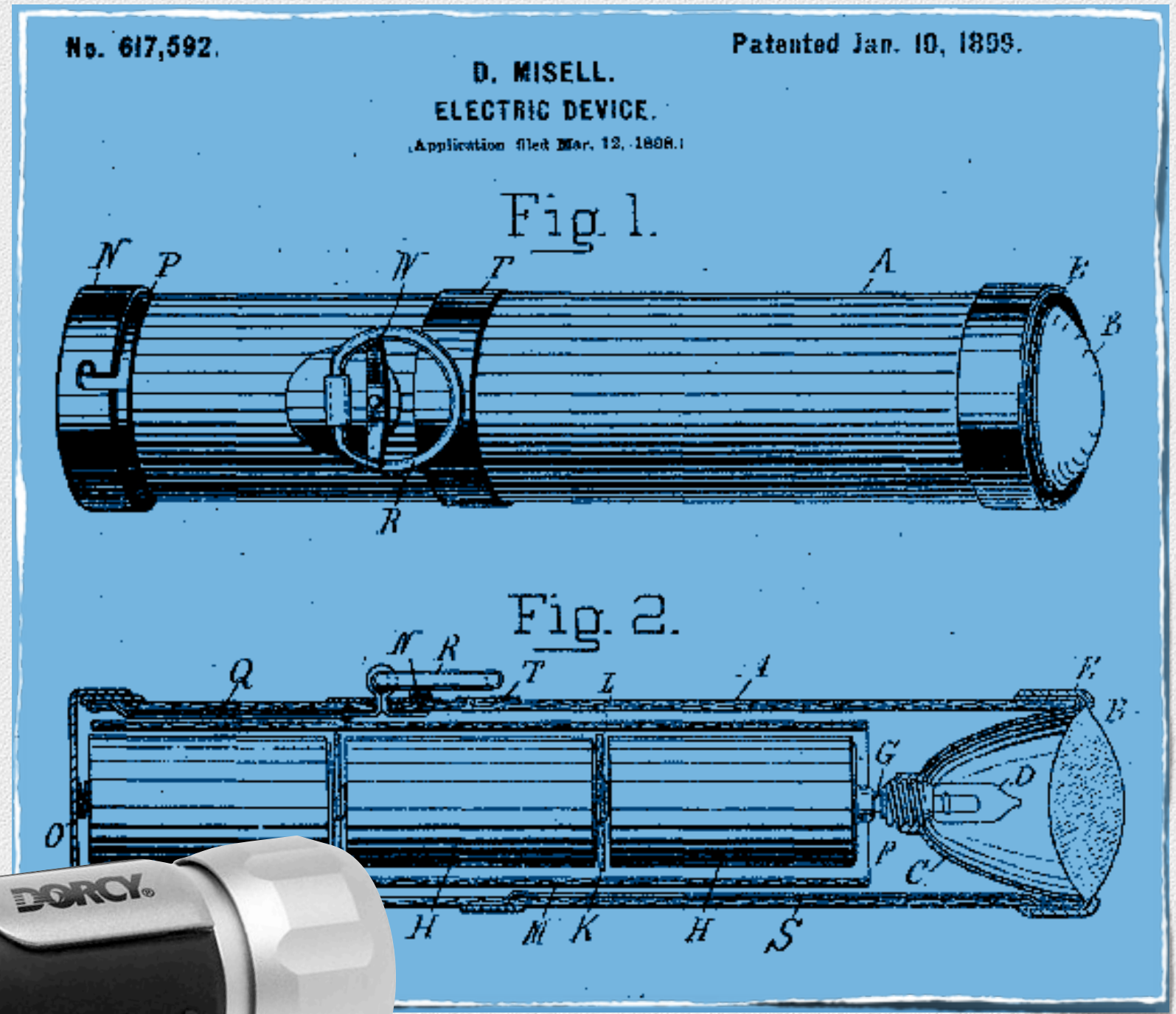


Why is a camera flash different?




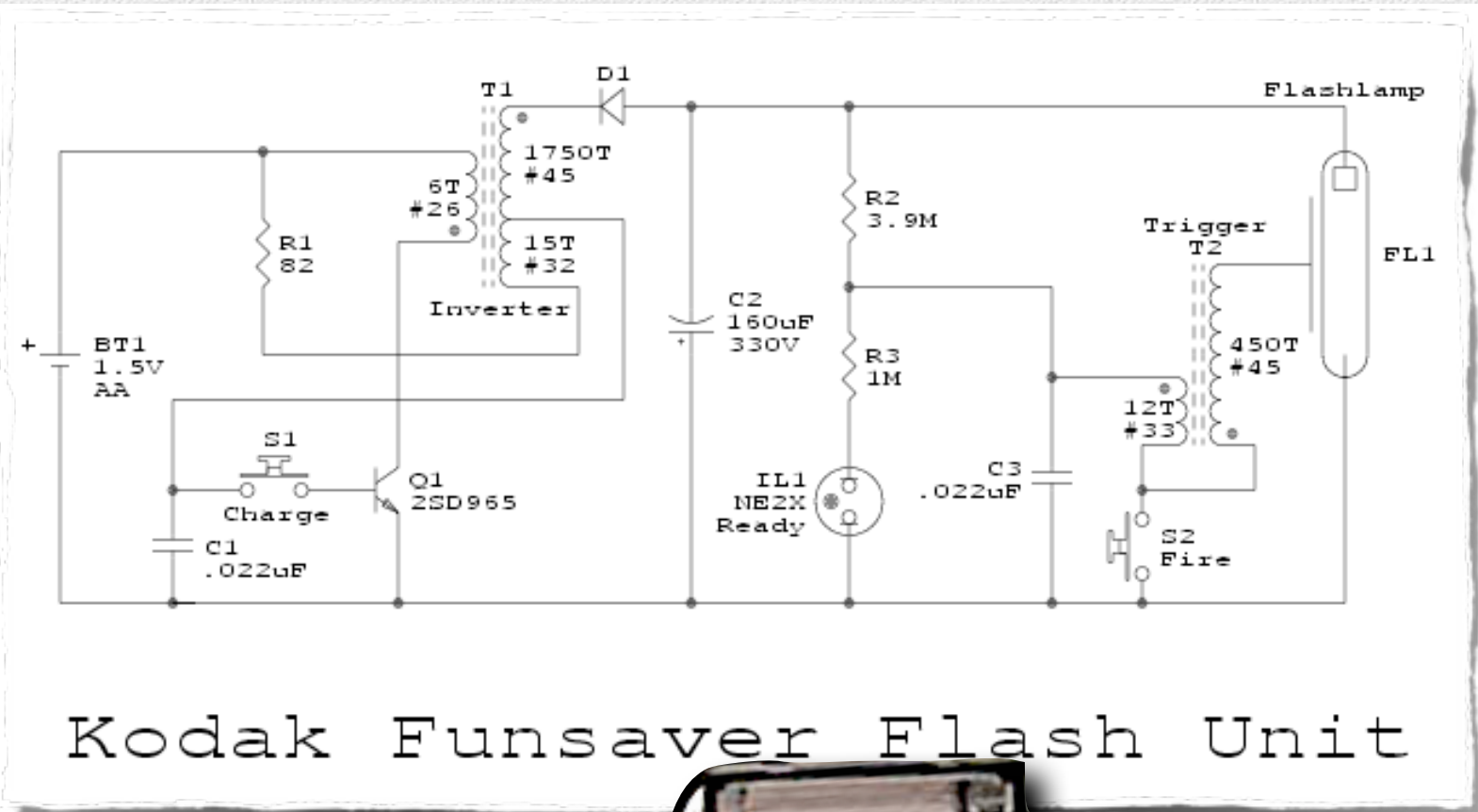

Capacitors

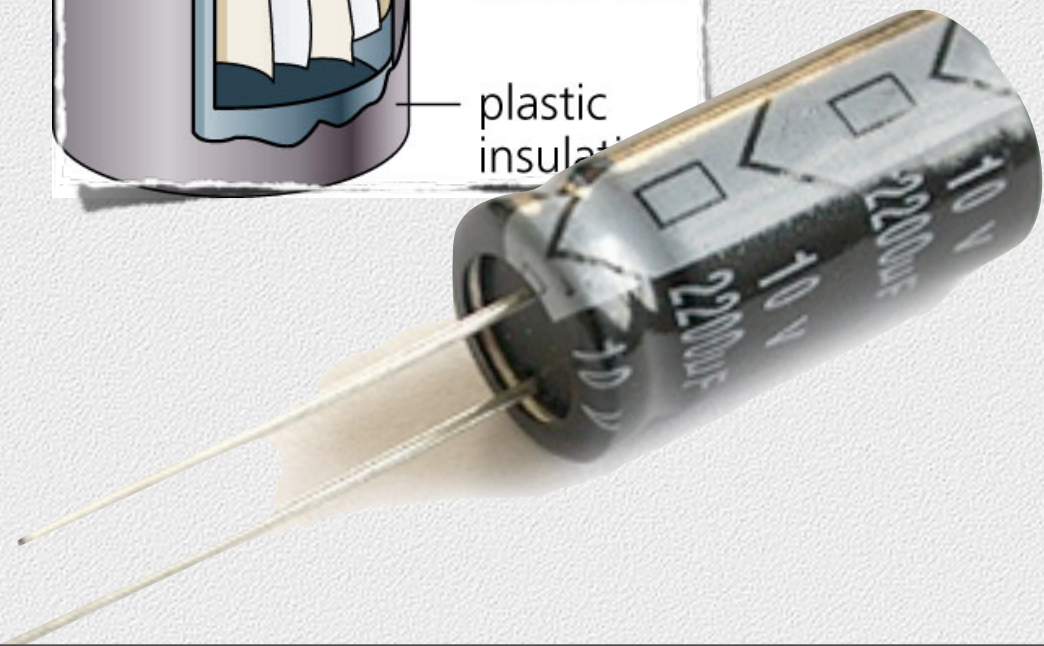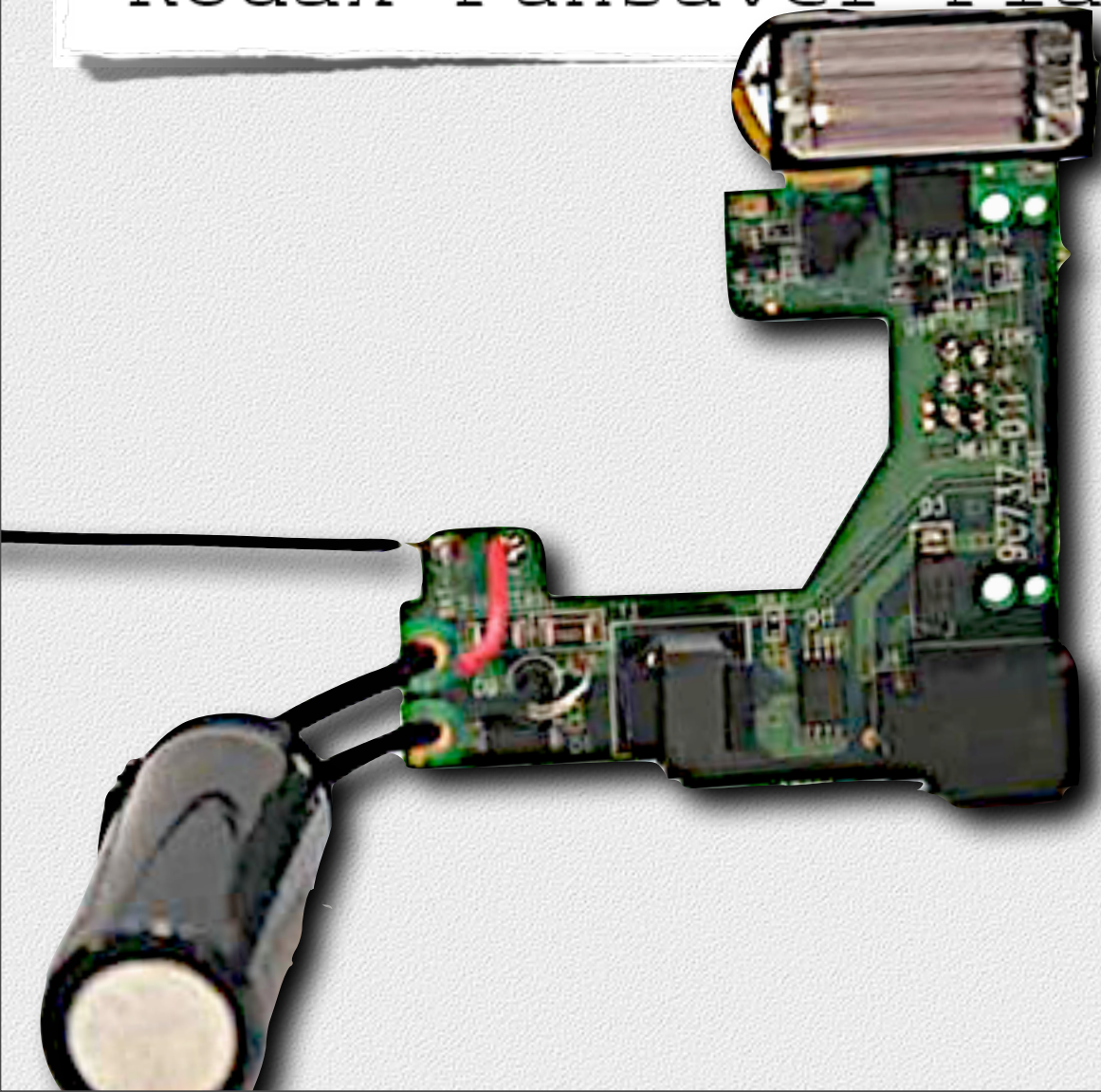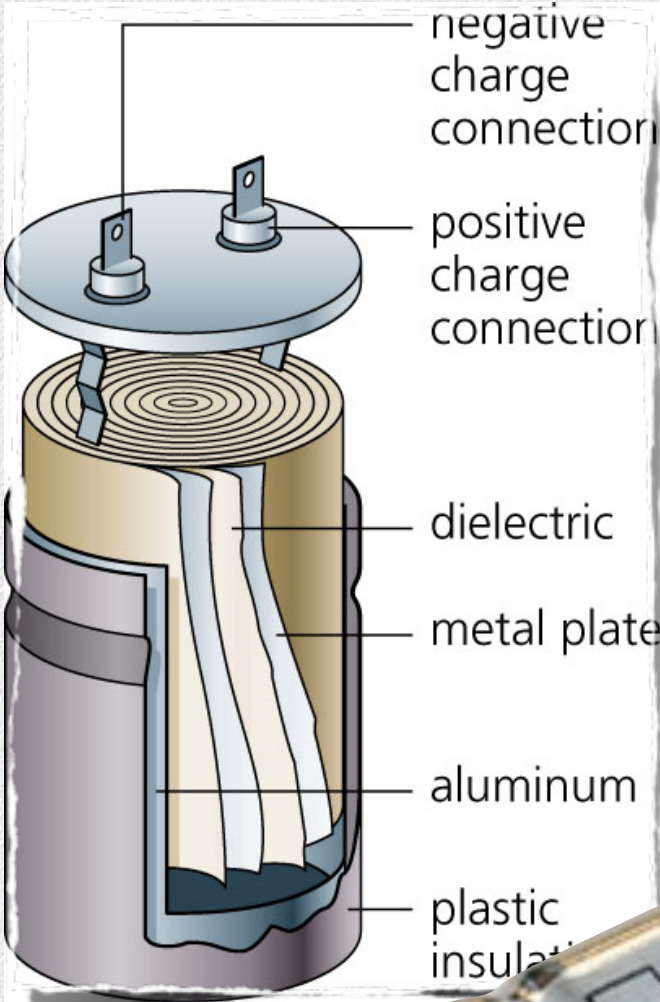

Unit - Farad

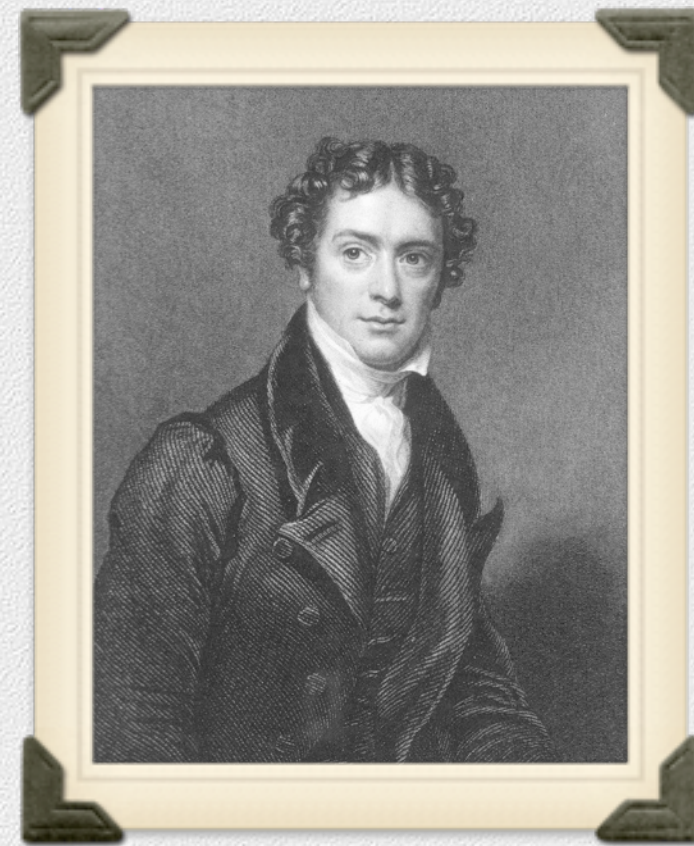

Michael
Faraday
1791-1867



$1\ \mu\text{F}$
Normal
Circuits



$1\ \text{F}$
A bit crazy

Capacitance

- C - Capacitance
 - Unit - Farad (F)
- Q - Charge
 - Unit - Coulomb (C)
- V - Potential or Voltage
 - Unit - Volt (V)

$$C = \frac{Q}{V}$$

$$Q = VC$$

Equations


$$W = \frac{1}{2}QV$$

- W - Work or Energy (Joule)
- combinations include;

$$W = \frac{1}{2}cv^2$$

$$W = \frac{1}{2} \frac{Q^2}{C}$$

Capacitors in Parallel

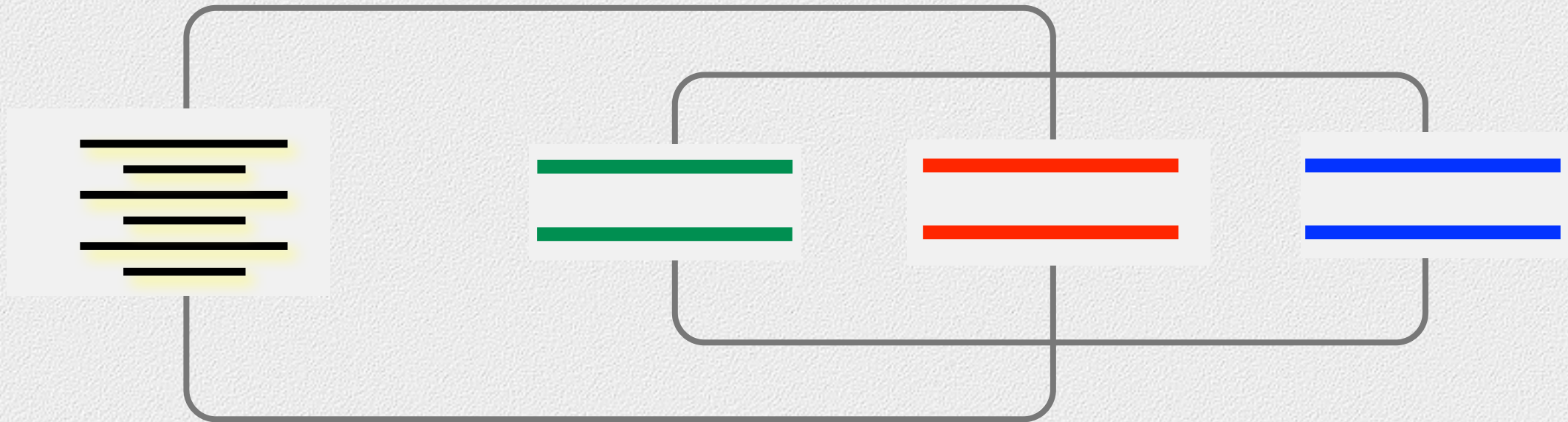

There is more room for the charges to be stored, making this a stronger total capacitance.

Voltage:

$$V_T = V_1 = V_2 = V_3$$


Charge:

$$Q_T = Q_1 + Q_2 + Q_3$$

Capacitance:


$$C_T = C_1 + C_2 + C_3$$

Capacitors in Parallel

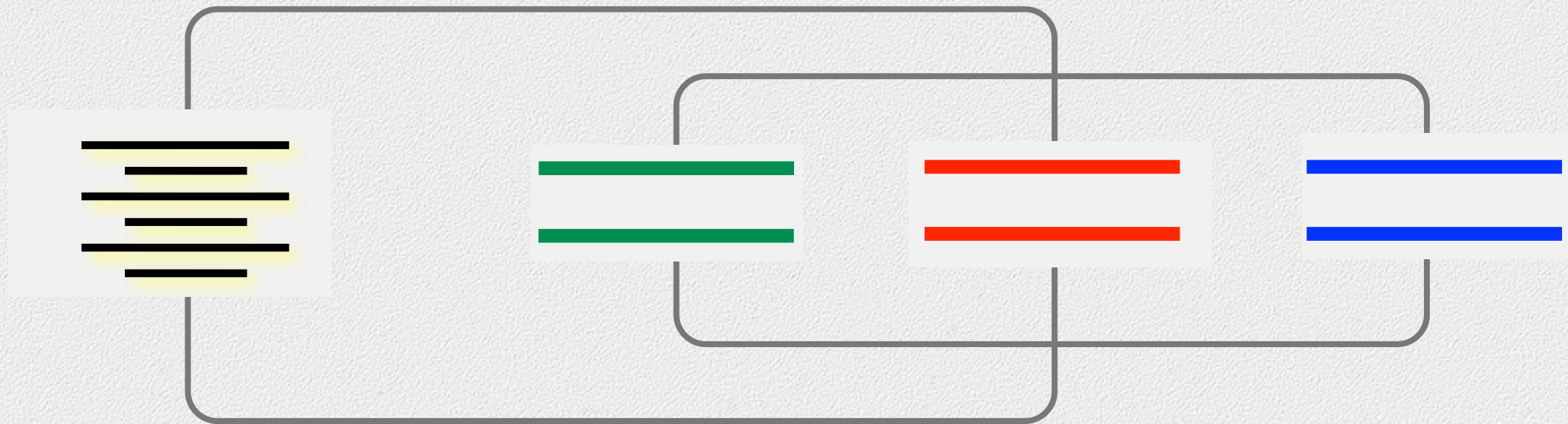


	Q (C)	V (V)	C (F)	W (J)
C_1			4	
C_2			6	
C_3			10	
TOTAL		10	20	

Capacitors in Parallel

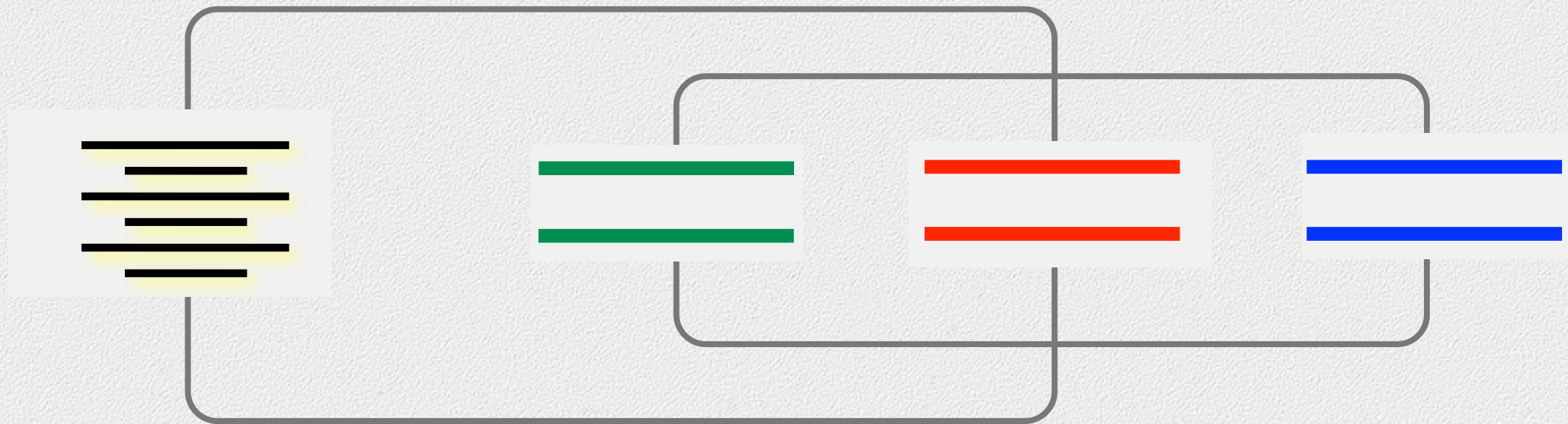


	Q (C)	V (V)	C (F)	W (J)
C_1		10	4	
C_2		10	6	
C_3		10	10	
TOTAL		10	20	

Capacitors in Parallel

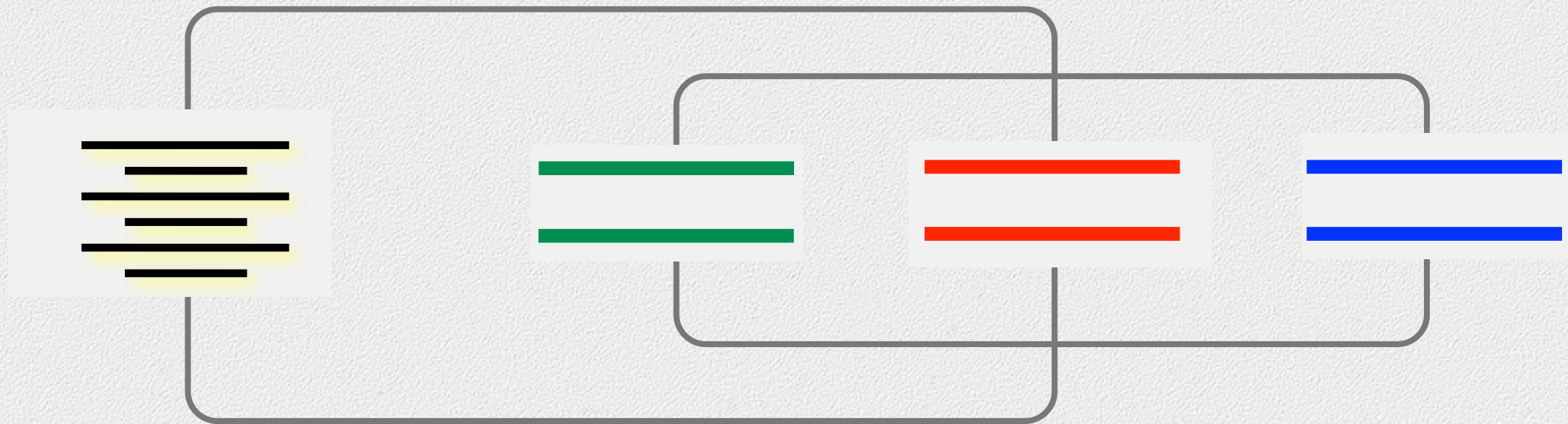


	Q (C)	V (V)	C (F)	W (J)
C_1	40	10	4	
C_2	60	10	6	
C_3	100	10	10	
TOTAL	200	10	20	

Capacitors in Parallel

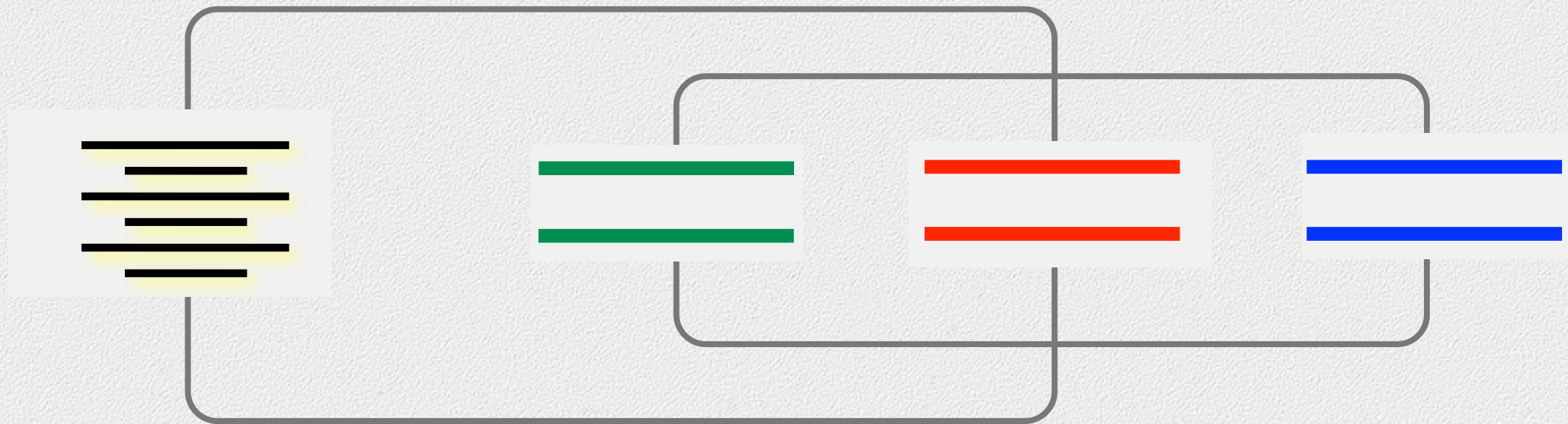

	Q (C)	V (V)	C (F)	W (J)
C_1	40	10	4	200
C_2	60	10	6	300
C_3	100	10	10	500
TOTAL	200	10	20	1000

Capacitors in Series

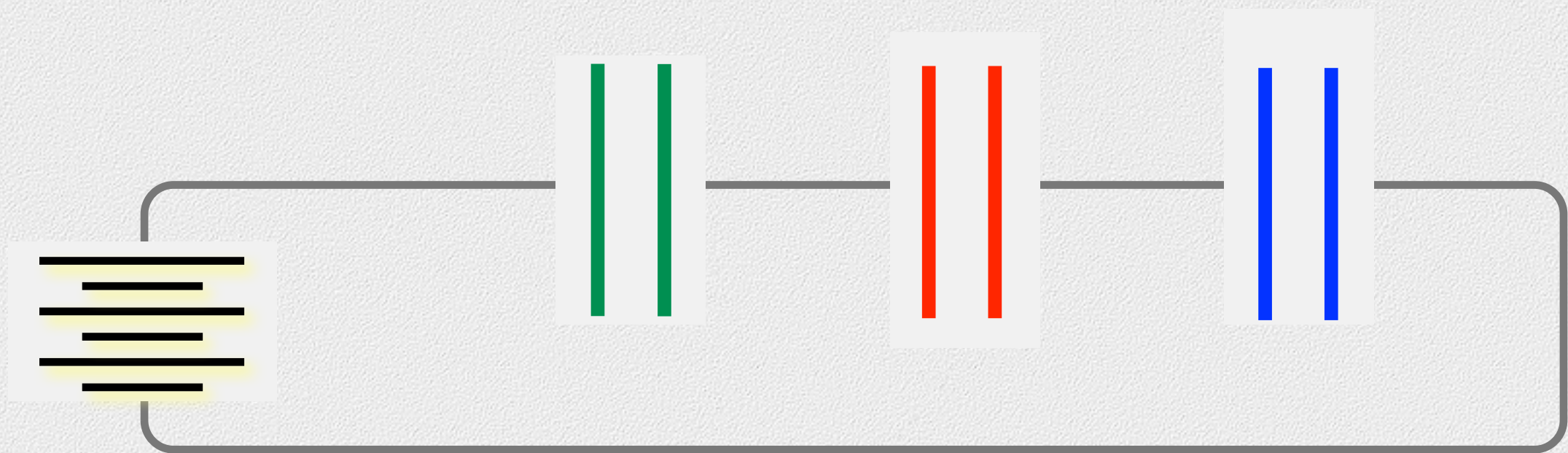


the source for potential is separated by even more distance, this decreases the charge that can be stored.

Voltage: $V_T = V_1 + V_2 + V_3$

Charge: $Q_T = Q_1 = Q_2 = Q_3$


Capacitance: $1/C_T = 1/C_1 + 1/C_2 + 1/C_3$

Capacitors in Series

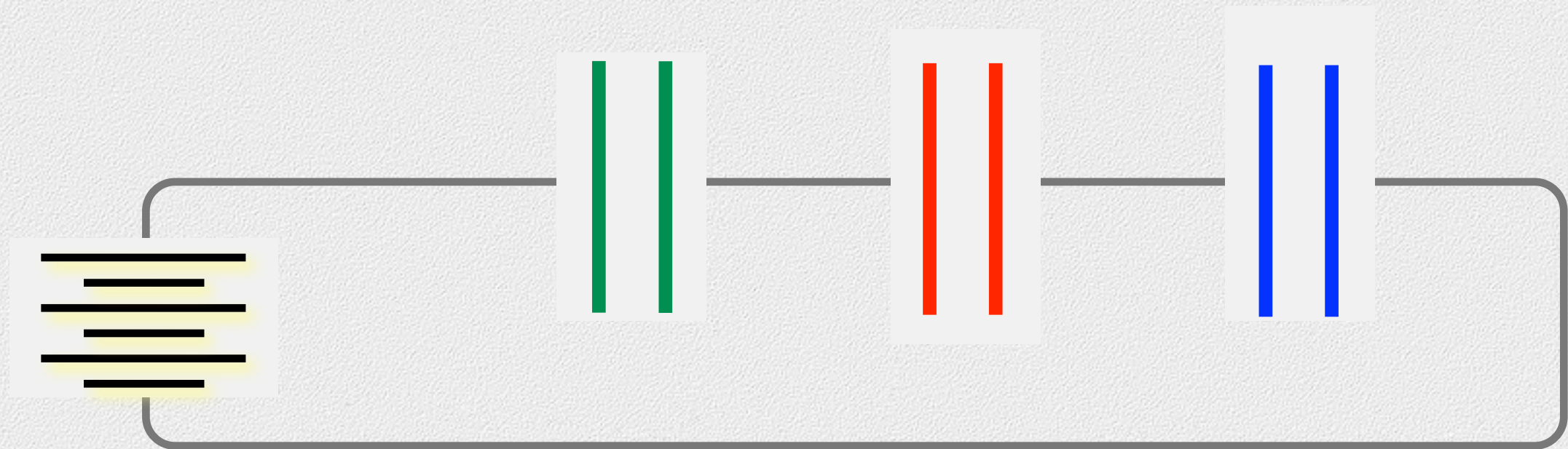


	Q (C)	V (V)	C (F)	W (J)
C_1			120	
C_2			30	
C_3			24	
TOTAL	1200	100	12	

Capacitors in Series

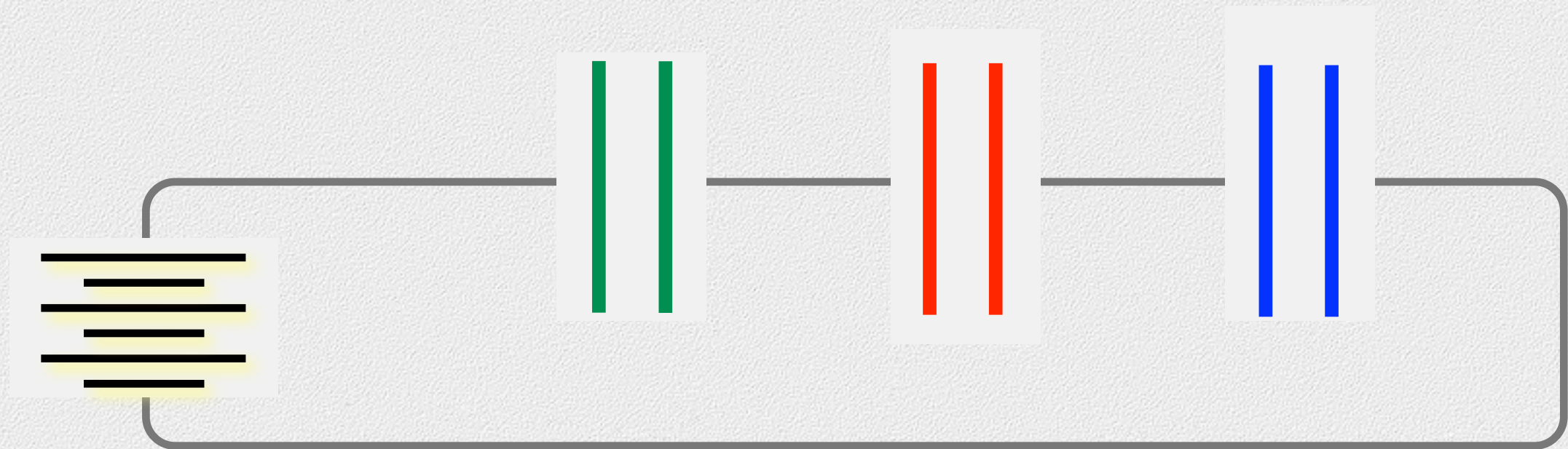


	Q (C)	V (V)	C (F)	W (J)
C_1	1200		120	
C_2	1200		30	
C_3	1200		24	
TOTAL	1200	100	12	

Capacitors in Series

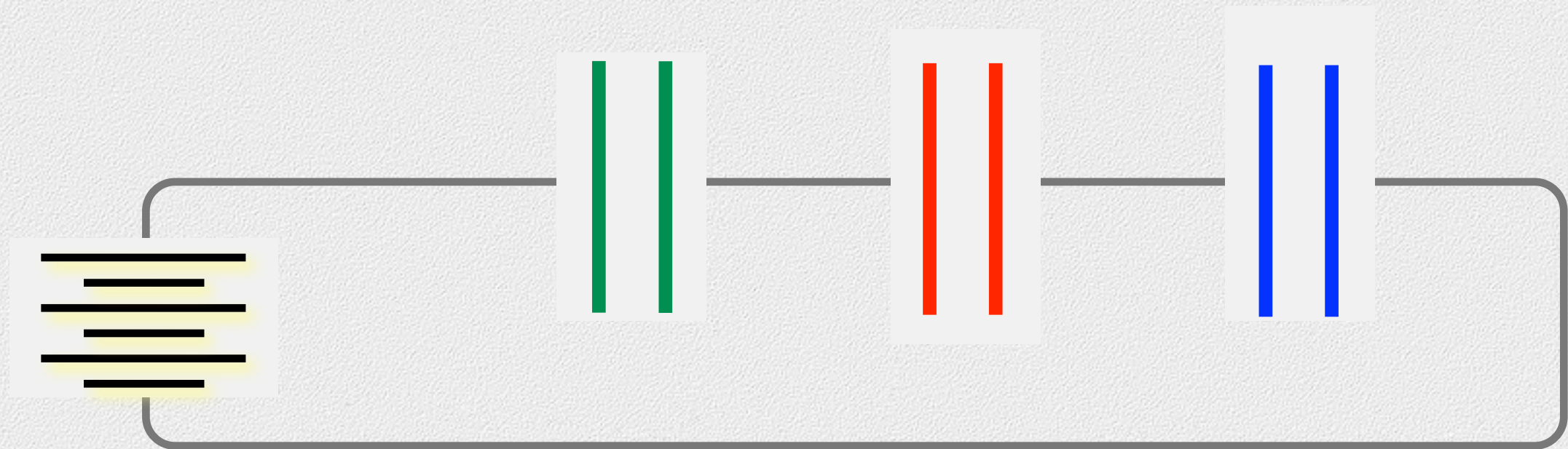

	Q (C)	V (V)	C (F)	W (J)
C_1	1200	10	120	
C_2	1200	40	30	
C_3	1200	50	24	
TOTAL	1200	100	12	


Capacitors in Series

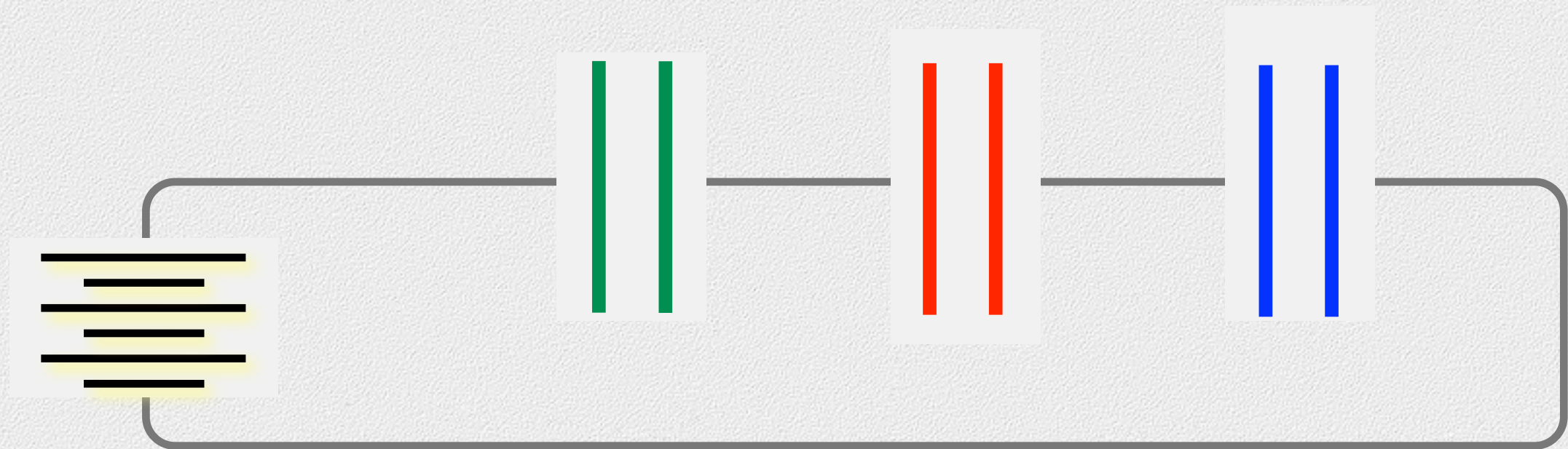

	Q (C)	V (V)	C (F)	W (J)
C_1	1200	10	120	6,000
C_2	1200	40	30	24,000
C_3	1200	50	24	30,000
TOTAL	1200	100	12	60,000

Capacitance

$$C = \frac{k\epsilon_o A}{d}$$

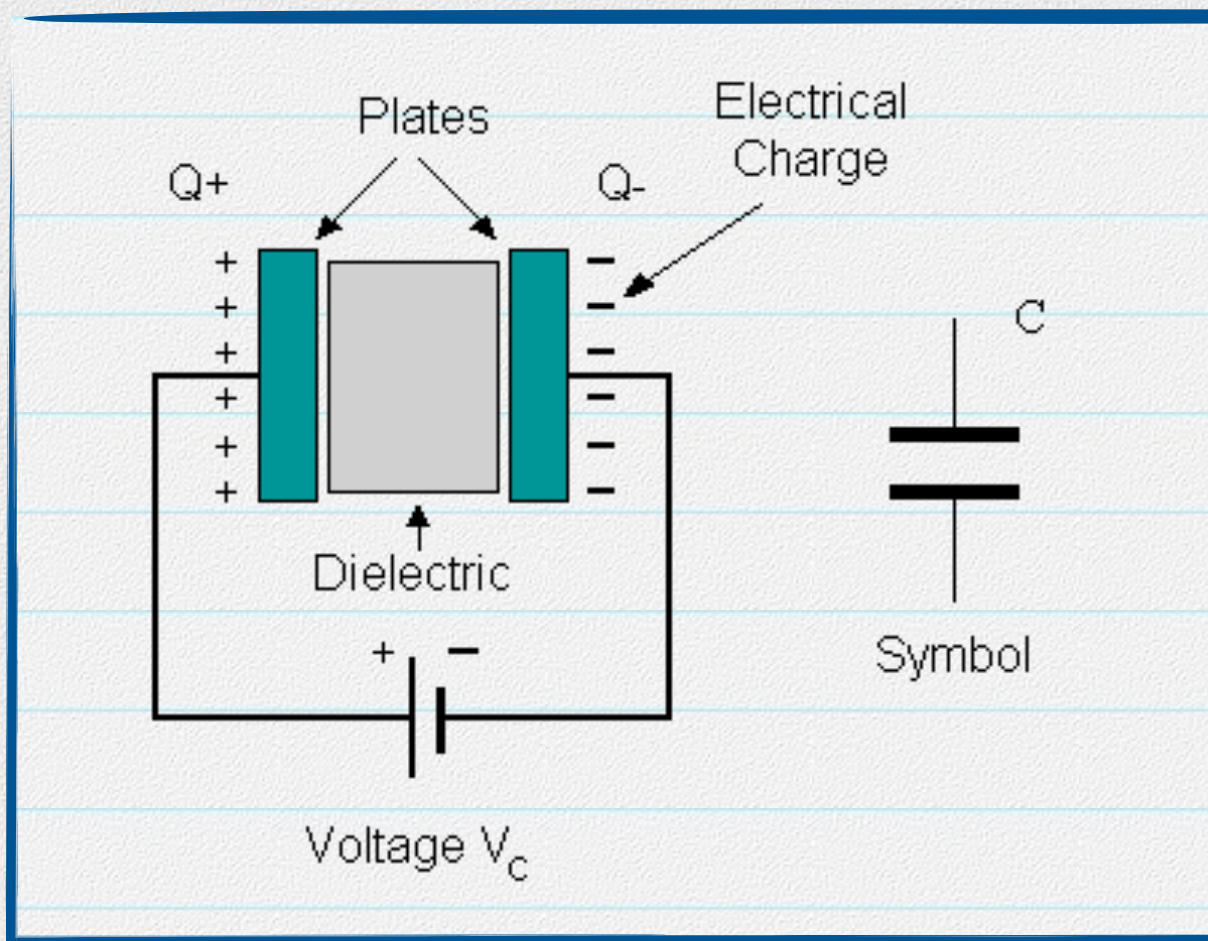

- Capacitance Farad (F)
- Permittivity of Free Space
 - $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$
 - k - Relative permittivity
 - Dielectric
- Area m^2
- Separation m