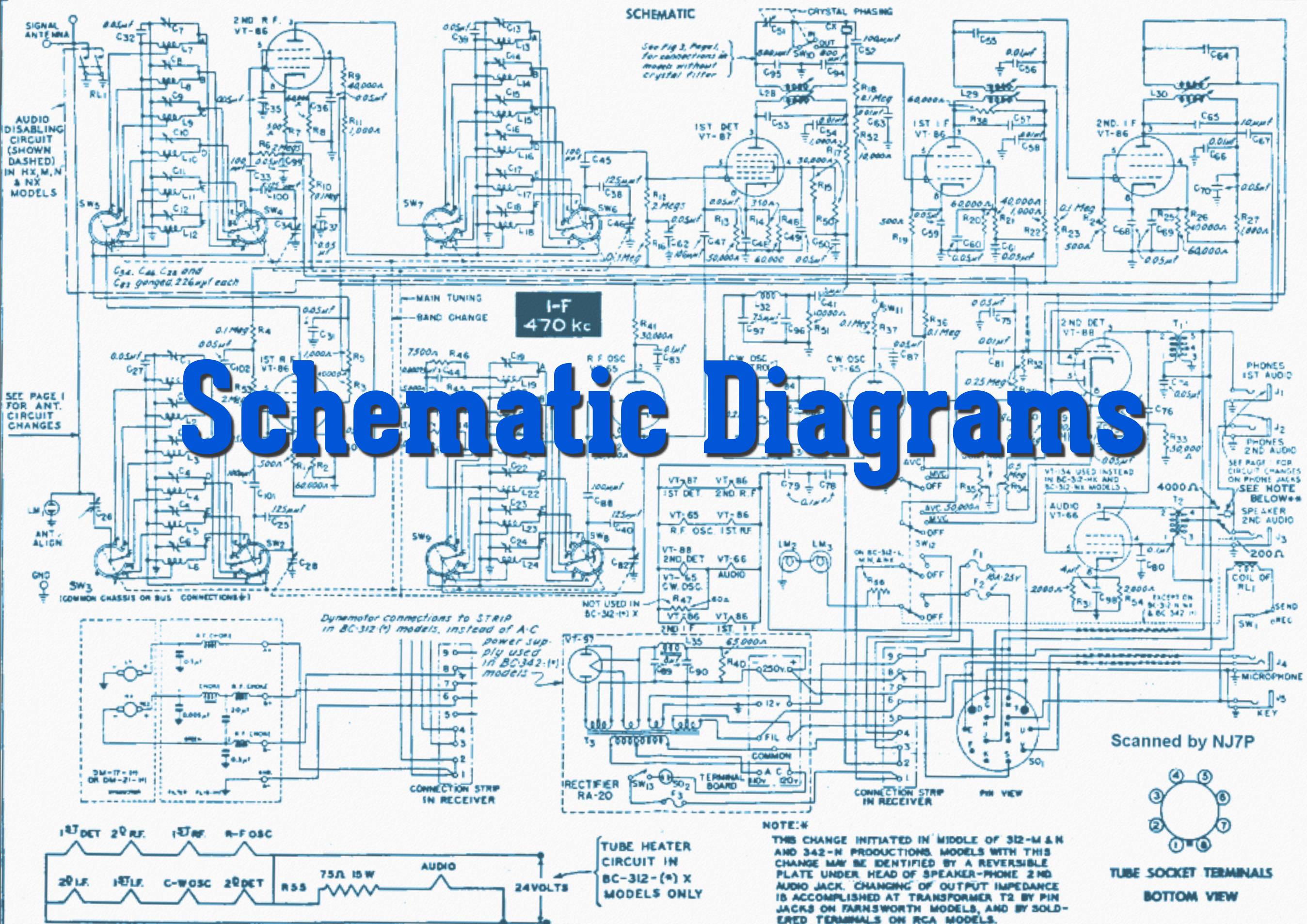


Electric Circuits






Scanned by NJ7P

TUBE SOCKET TERMINALS
BOTTOM VIEW


Schematic Icons

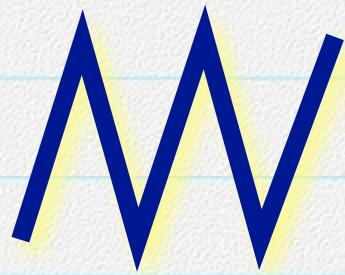


Resistor



Switch

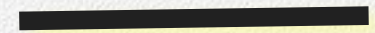

Wire

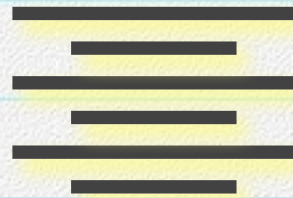

Battery



Light Bulb

Resistance

$$R = \frac{\rho L}{A}$$


- Resistance Ω
- resistivity Ωm
- length m
- area m^2

Table 20.1 Resistivities of Various Materials

Material	Resistivity ρ ($\Omega \cdot \text{m}$)	Material	Resistivity ρ ($\Omega \cdot \text{m}$)
Conductors		Semiconductors	
Aluminum	2.82×10^{-8}	Carbon	3.5×10^{-5}
Copper	1.72×10^{-8}	Germanium	0.5^b
Gold	2.44×10^{-8}	Silicon	$20\text{--}2300^b$
Iron	9.7×10^{-8}	Insulators	
Mercury	95.8×10^{-8}	Mica	$10^{11}\text{--}10^{15}$
Nichrome (alloy)	100×10^{-8}	Rubber (hard)	$10^{13}\text{--}10^{16}$
Silver	1.59×10^{-8}	Teflon	10^{16}
Tungsten	5.6×10^{-8}	Wood (maple)	3×10^{10}


The values pertain to temperatures near 20 °C.

^a Purity.

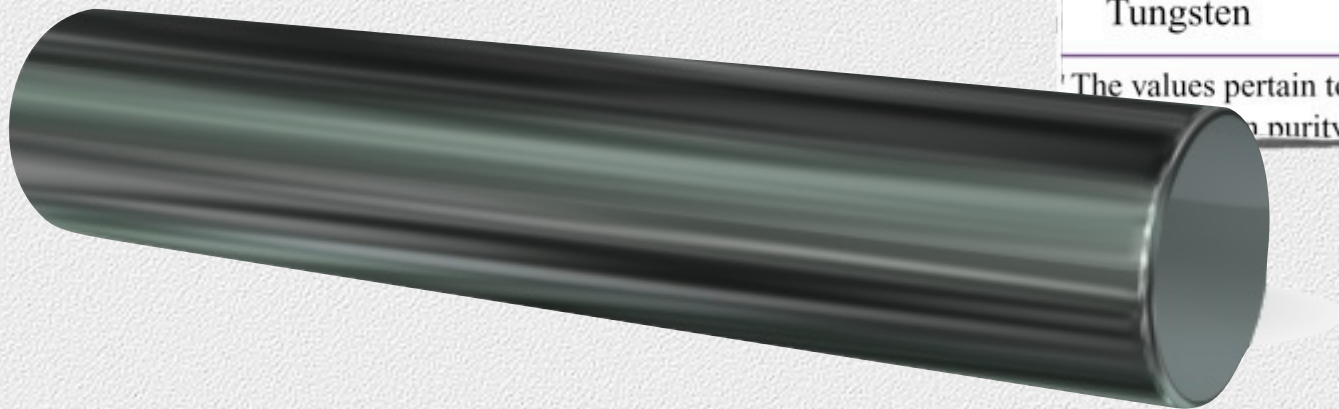



Georg Simon Ohm
1789-1854

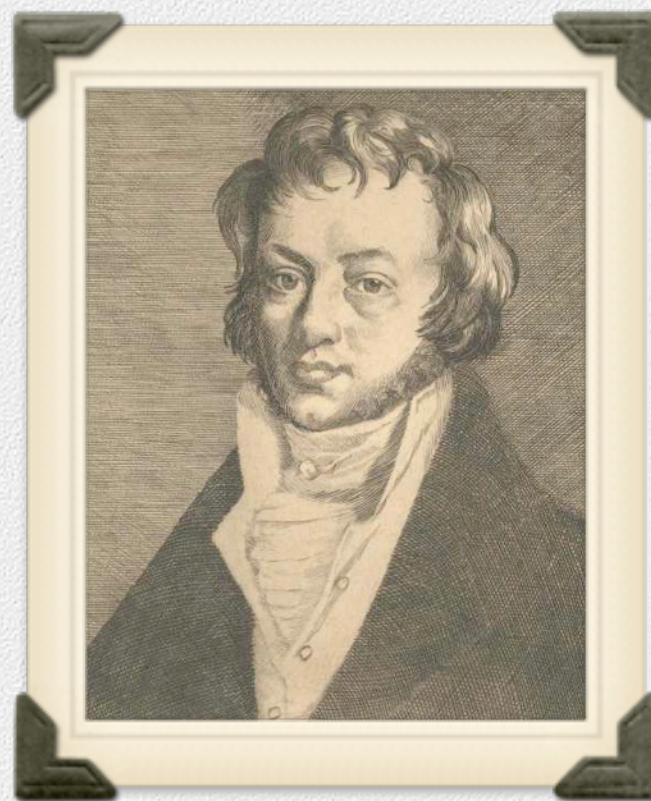

André-Marie Ampère
1775-1836



Alessandro Giuseppe Antonio Anastasio Gerolamo Umberto Volta
1745-1827

Ohm's Law

$$V = I R$$

$$\mathcal{E} = I R$$

Potential or
Voltage (**V**) in Volts (**V**)

Current (**I**) in Amperes (**A**)


Resistance (**R**) in Ohms (Ω)



Charles-Augustin
de Coulomb
1736-1806

- The charge of a single electron is 1.6021×10^{-19} Coulombs
- or... it would take 6.241×10^{18} electrons to have a Coulomb of charge
- 1 Ampere is a current of that many electrons every second.

Electric Charge

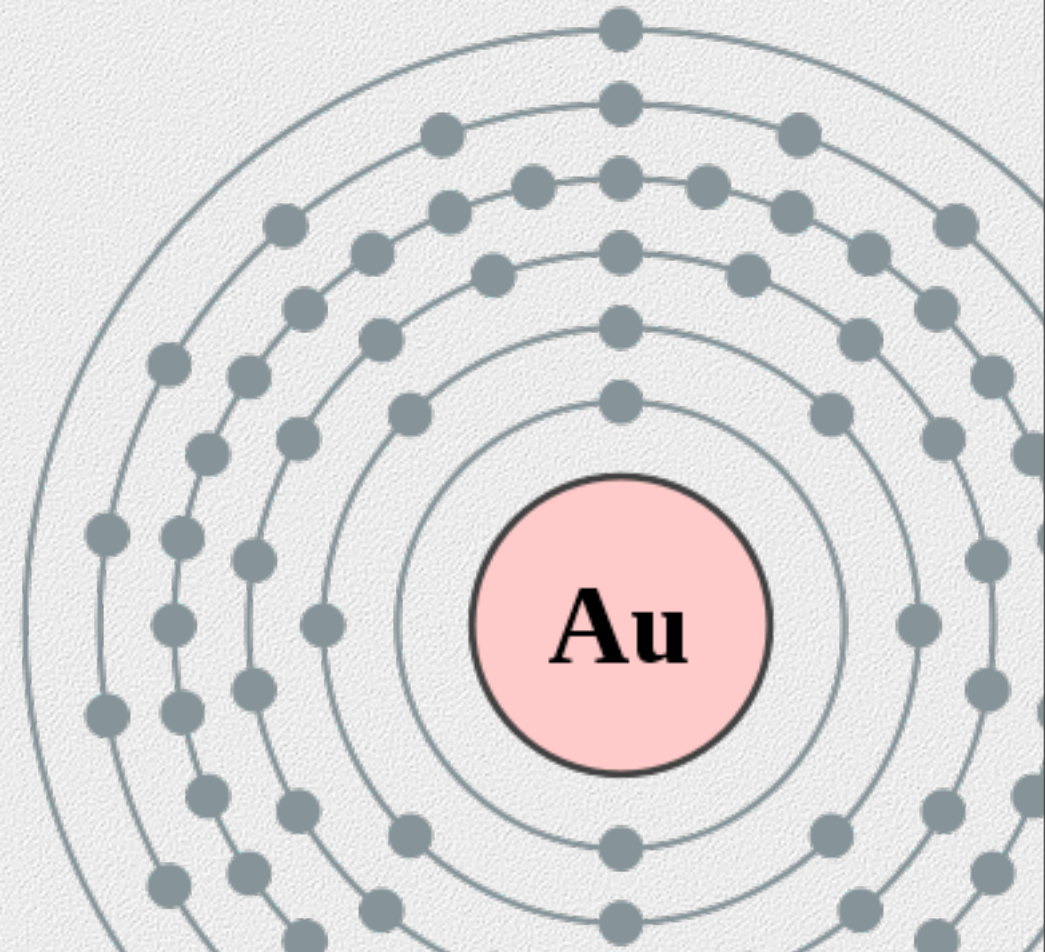


Power


$$P = IV$$

$$P = V^2/R$$

$$P = I^2R$$

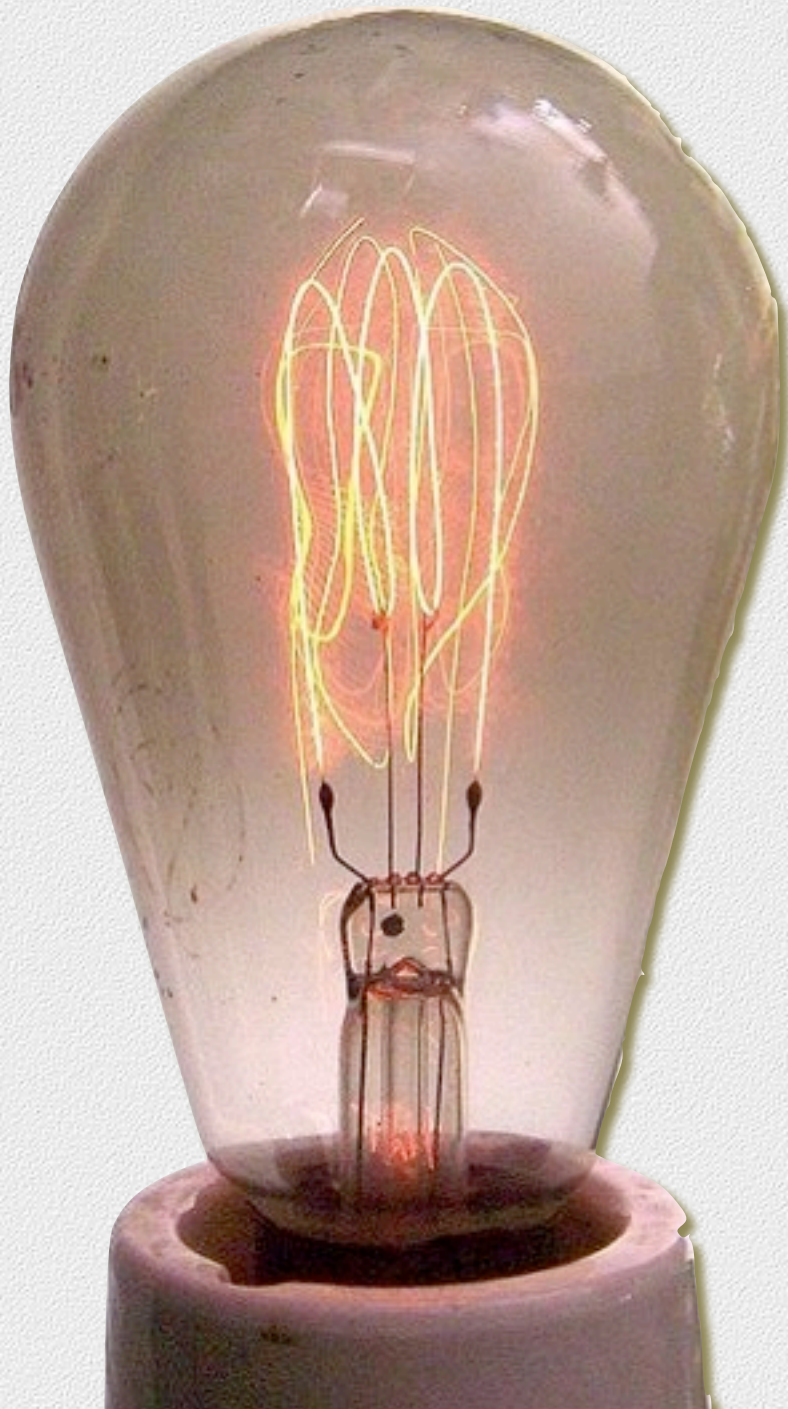

Resistors in Series

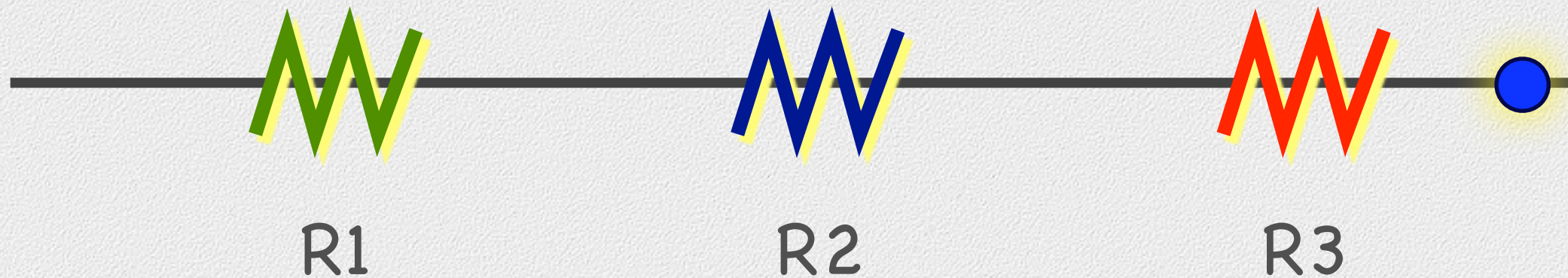


- The Charges have to “fight” through every resistor. This decreases the total current.

Voltage: $V_T = V_1 + V_2 + V_3$

Current: $I_T = I_1 = I_2 = I_3$

Resistance: $R_T = R_1 + R_2 + R_3$


Series

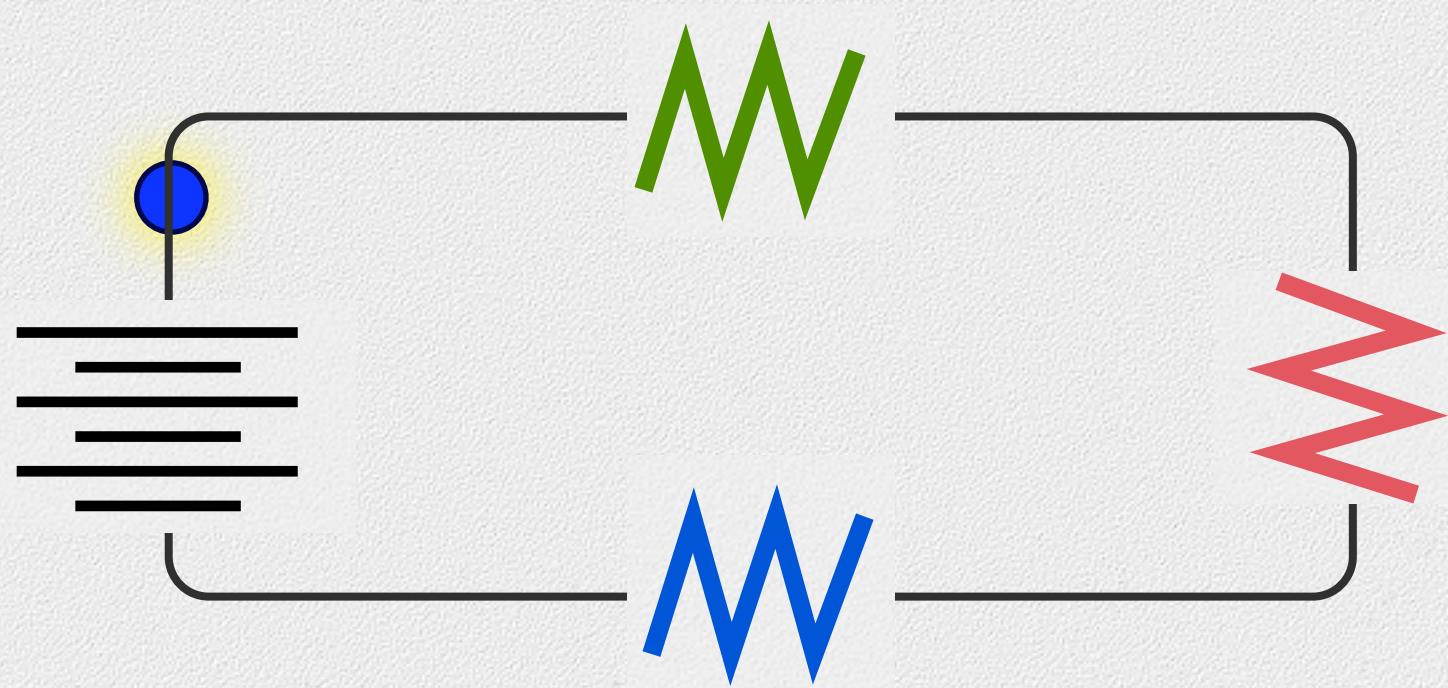

The current starts at the top of the battery and follows a single path, clockwise, around the circuit.

	V (V)	I (A)	R (Ω)	P (W)
R₁			2	
R₂			4	
R₃			6	
TOTAL	24			


Series

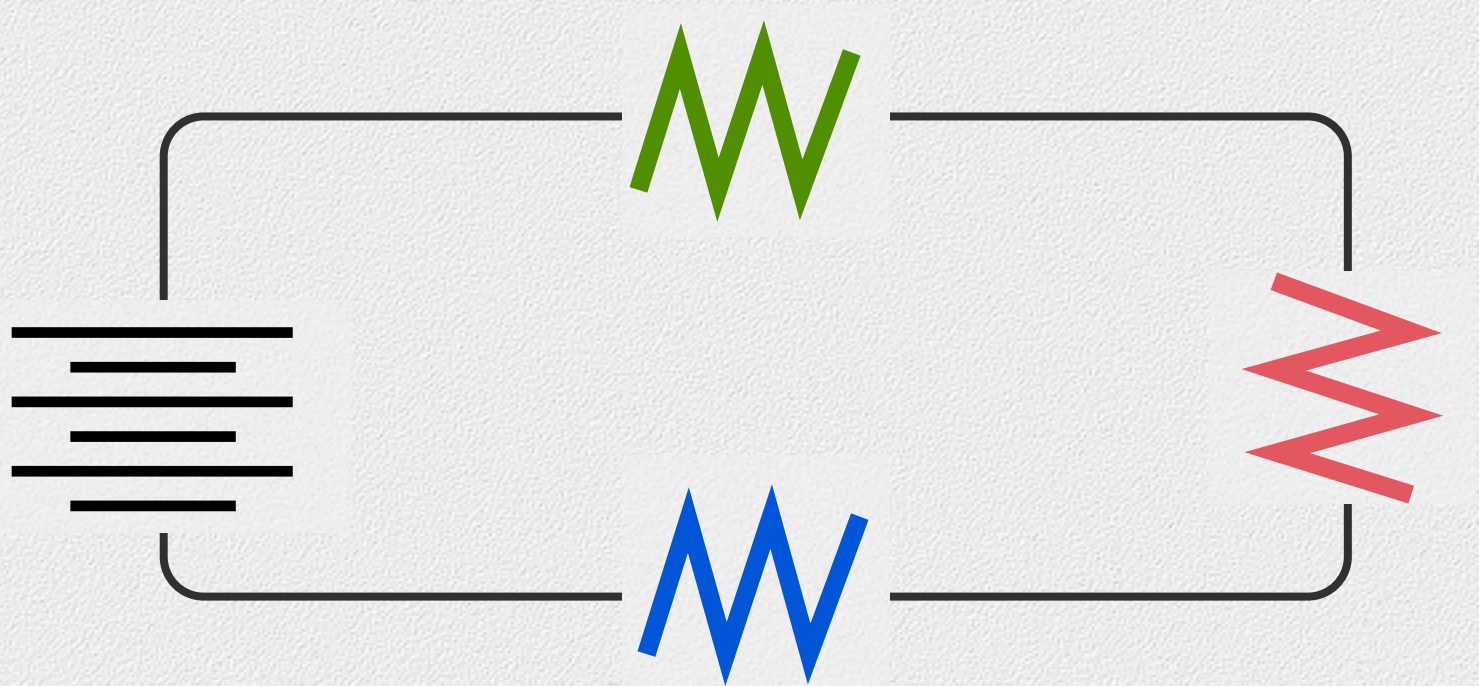

Start with the total resistance, a simple sum of the individual values

	V (V)	I (A)	R (Ω)	P (W)
R_1			2	
R_2			4	
R_3			6	
TOTAL	24		12	

Series

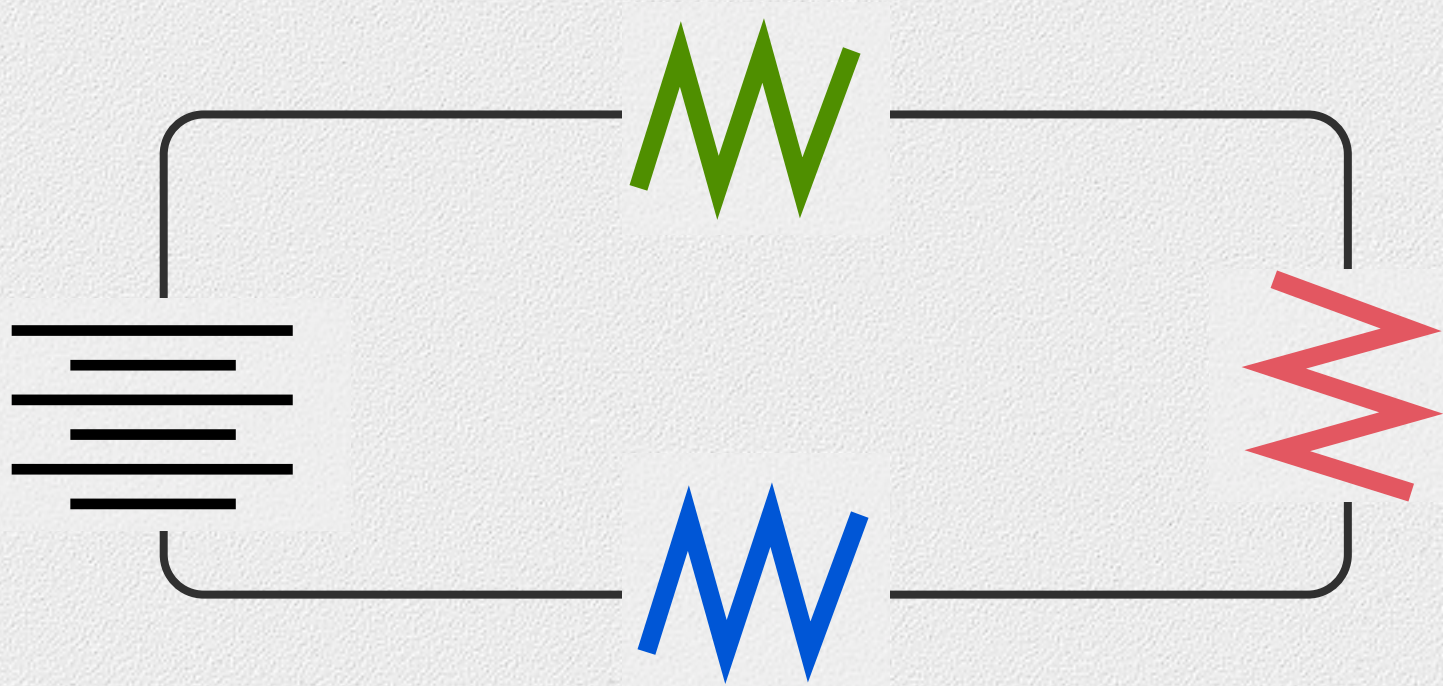


Use the total resistance to find the total current.

$$\begin{aligned} I &= V / R \\ &= 24 / 12 \\ &= 2 \text{ Amperes} \end{aligned}$$

	V (V)	I (A)	R (Ω)	P (W)
R_1			2	
R_2			4	
R_3			6	
TOTAL	24	2	12	


Series

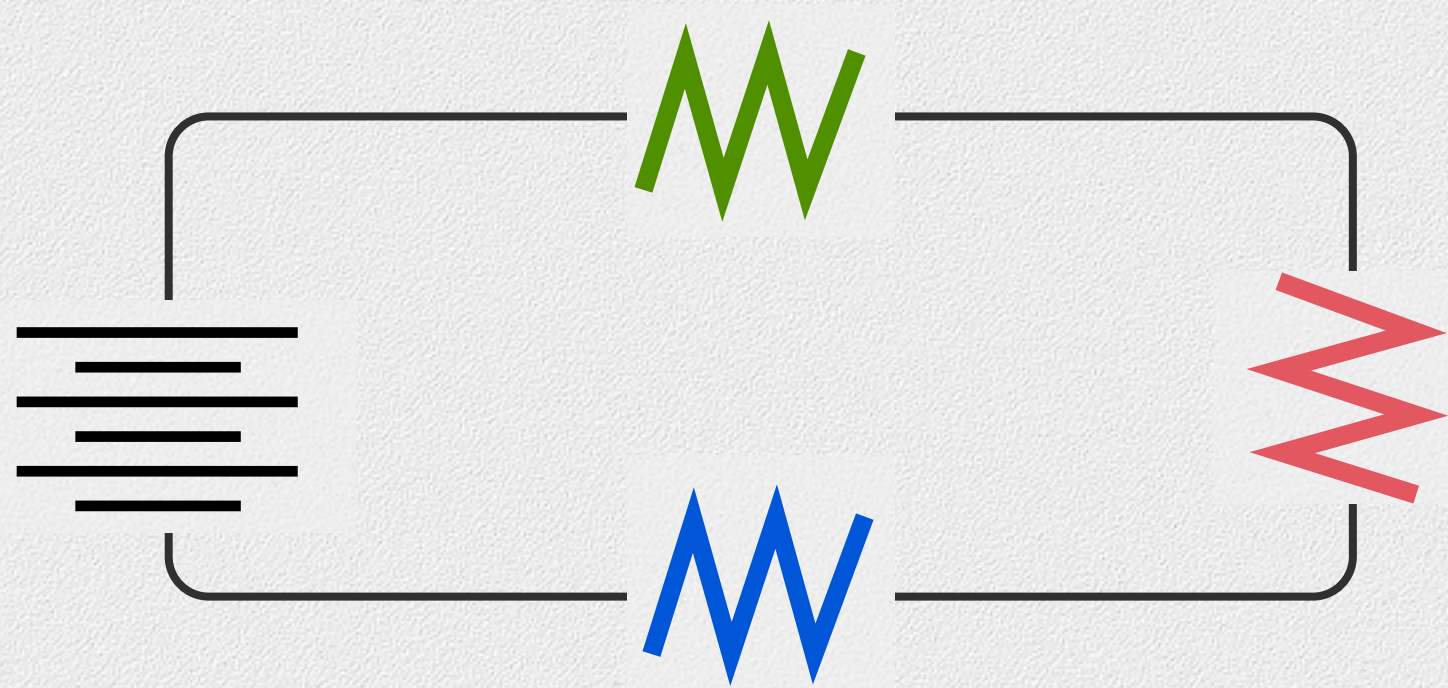

In a series circuit, there is only one current, so that value can be applied to each resistor.

	V (V)	I (A)	R (Ω)	P (W)
R_1		2	2	
R_2		2	4	
R_3		2	6	
TOTAL	24	2	12	

Series

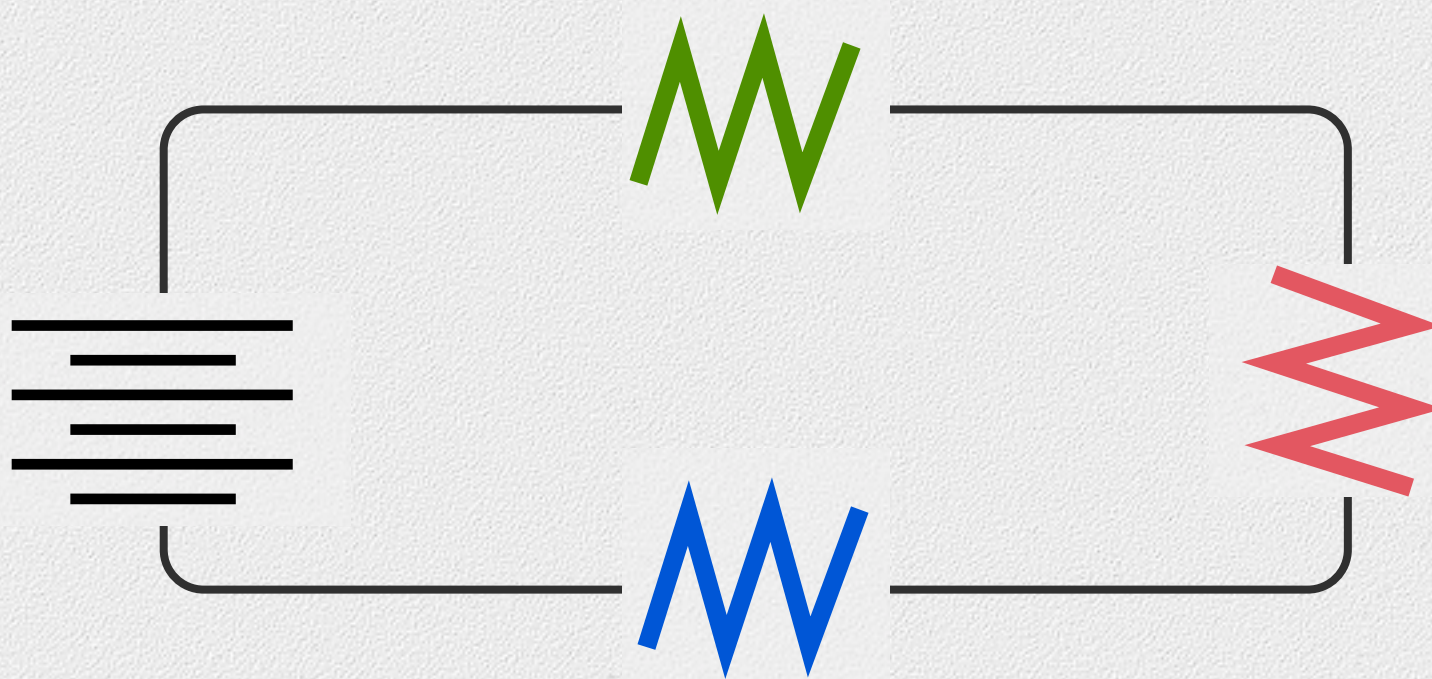


When you have two values for a resistor, equations will get you the other numbers.

$$V = I R$$

$$V_1 = 2 \times 2 = 4 \text{ Volts}$$

	V (V)	I (A)	R (Ω)	P (W)
R_1	4	2	2	
R_2	8	2	4	
R_3	12	2	6	
TOTAL	24	2	12	

Series

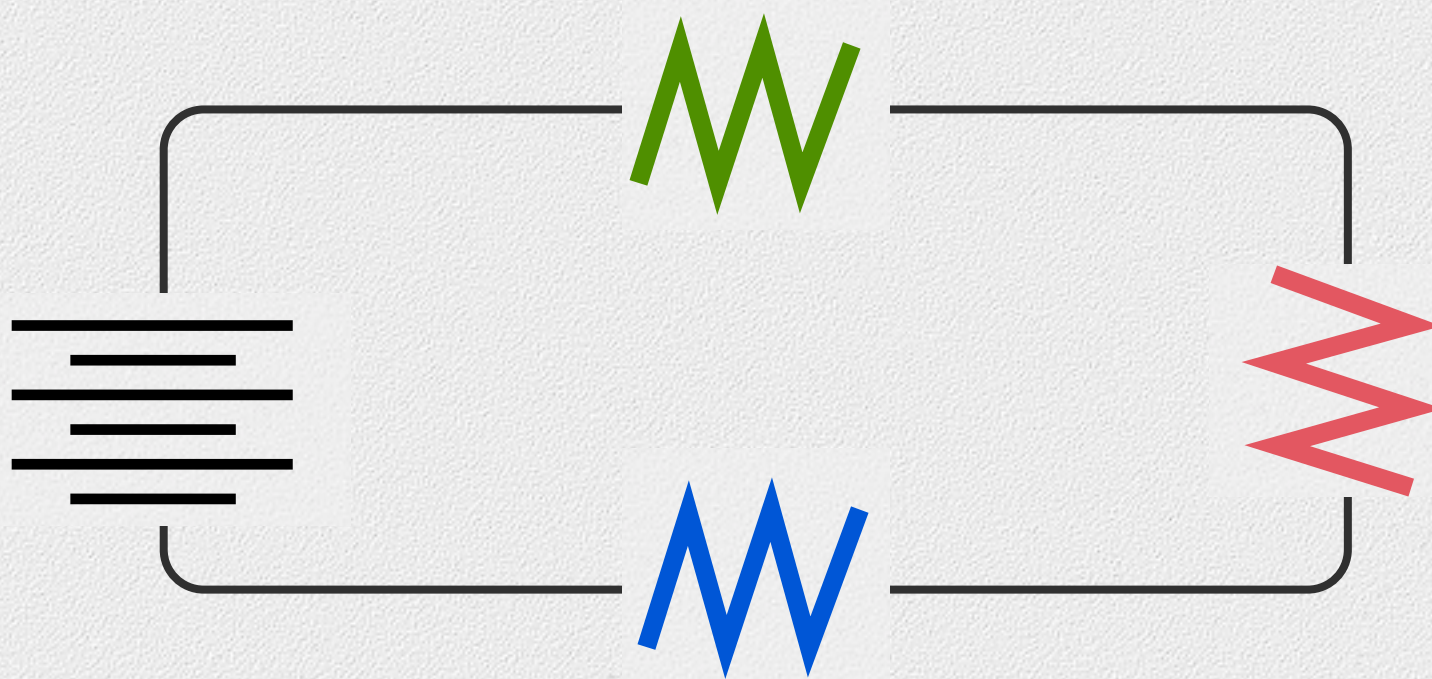


Save Power for last.
The sum should always
equal the product.

$$P = I V$$

$$P_{\text{Total}} = 24 \times 2 = 48 \text{ Watts}$$

	V (V)	I (A)	R (Ω)	P (W)
R_1	4	2	2	8
R_2	8	2	4	16
R_3	12	2	6	24
TOTAL	24	2	12	48

Resistors in Parallel

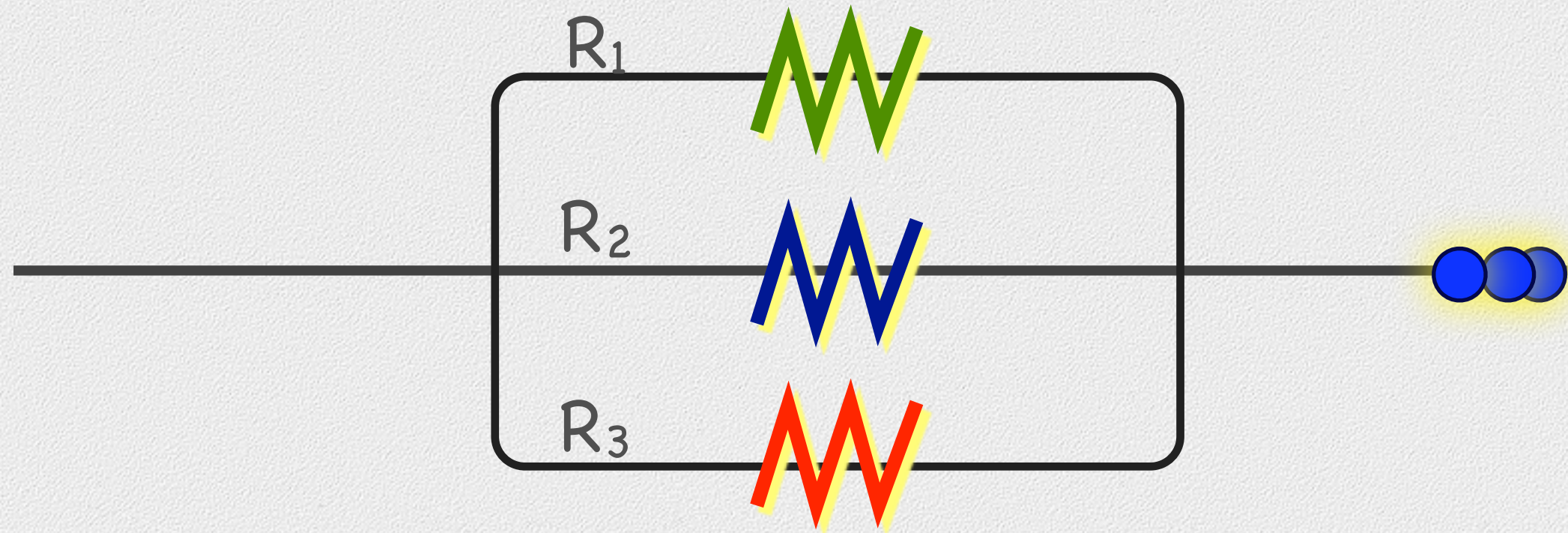


- The Charges have a choice of paths to follow.
- This decreases the total resistance.

Voltage: $V_T = V_1 = V_2 = V_3$

Current: $I_T = I_1 + I_2 + I_3$

Resistance: $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$

Parallel

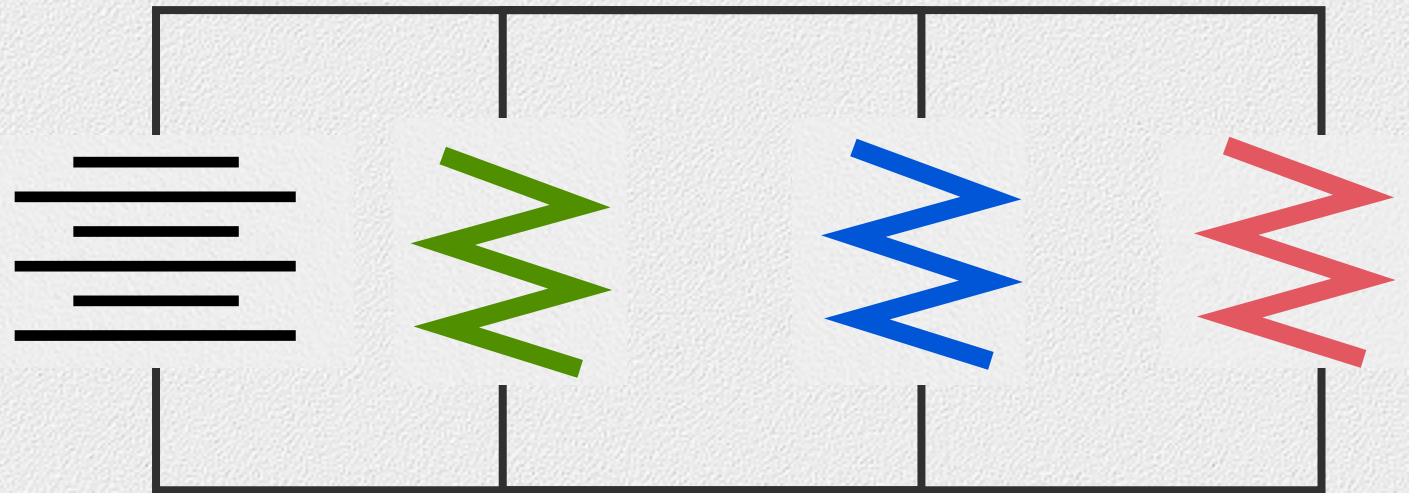

Add the resistors
inversely.


$$1/R_T = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_T = 1/120 + 1/60 + 1/10$$

$$R_T = 8 \, \Omega$$

	V (V)	I (A)	R (Ω)	P (W)
R ₁			120	
R ₂			60	
R ₃			10	
TOTAL	12		8	


Parallel

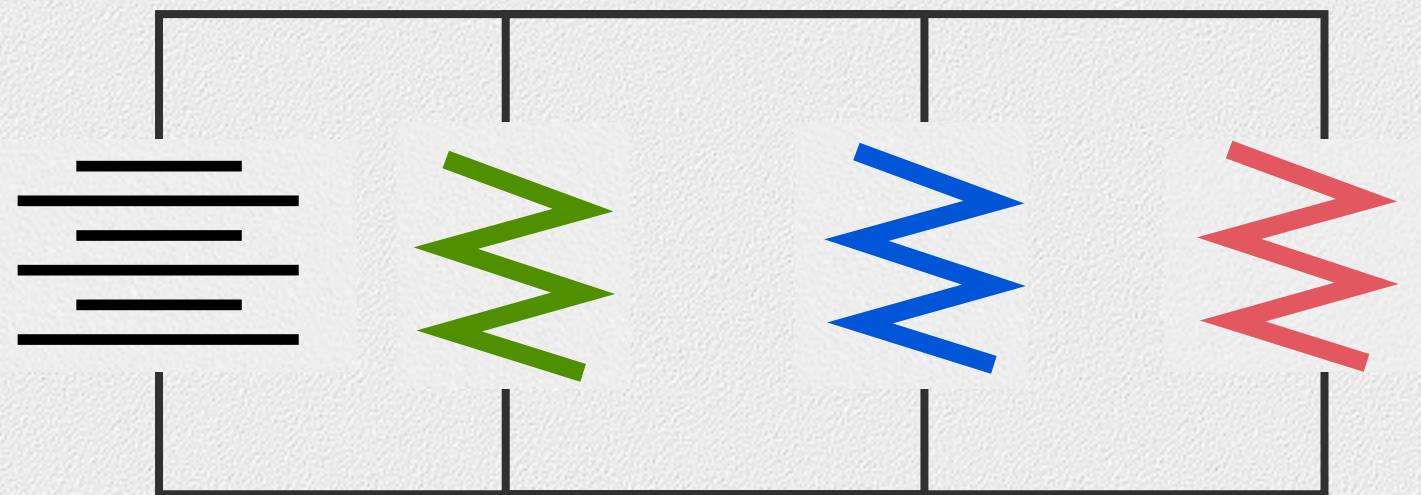

If you are given the total Voltage [EMF], resistors in parallel all have the same Voltage.

	V (V)	I (A)	R (Ω)	P (W)
R ₁	12		120	
R ₂	12		60	
R ₃	12		10	
TOTAL	12		8	

Parallel

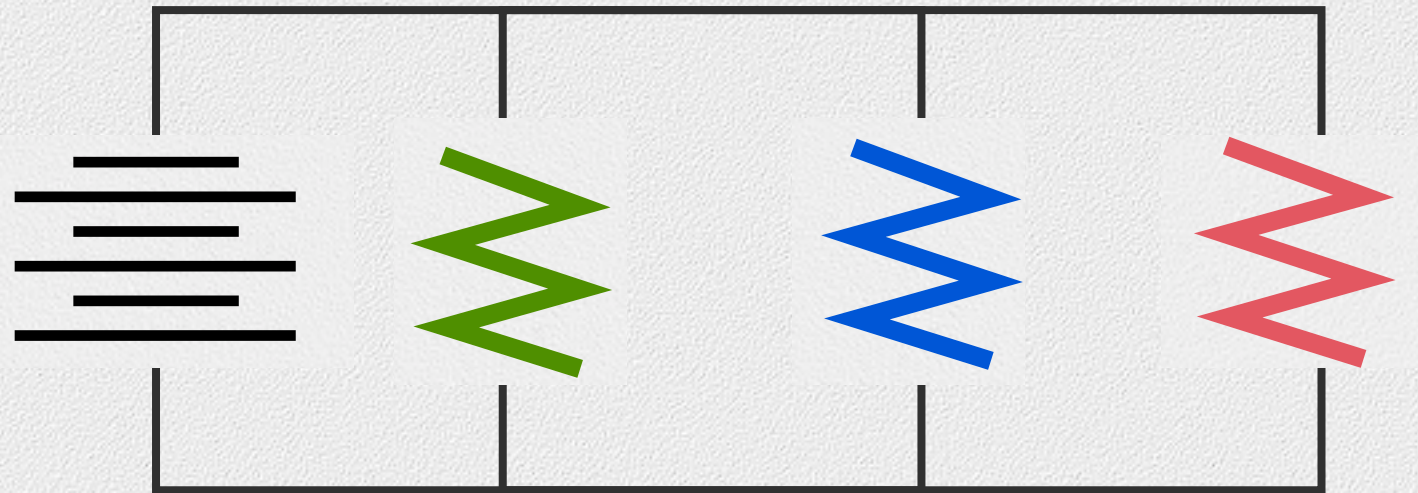

Use Ohm's Law to
find the currents


$$V = I R$$

$$12 = I_1 \times 120$$

$$I_1 = 0.1 \text{ Amperes}$$

	V (V)	I (A)	R (Ω)	P (W)
R ₁	12	0.1	120	
R ₂	12	0.2	60	
R ₃	12	1.2	10	
TOTAL	12	1.5	8	

Parallel

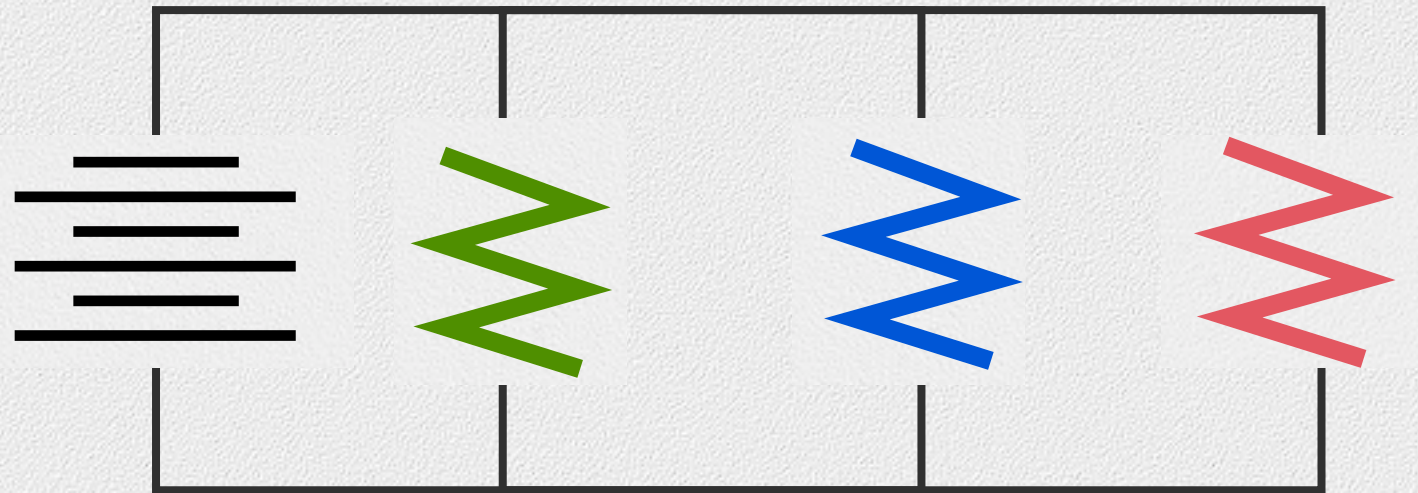

Multiply V and I to
find Power.


$$P = I V$$

$$P_1 = 0.1 \times 12$$

$$P_1 = 1.2 \text{ Watts}$$


	V (V)	I (A)	R (Ω)	P (W)
R ₁	12	0.1	120	1.2
R ₂	12	0.2	60	2.4
R ₃	12	1.2	10	14.4
TOTAL	12	1.5	8	18

Combinations

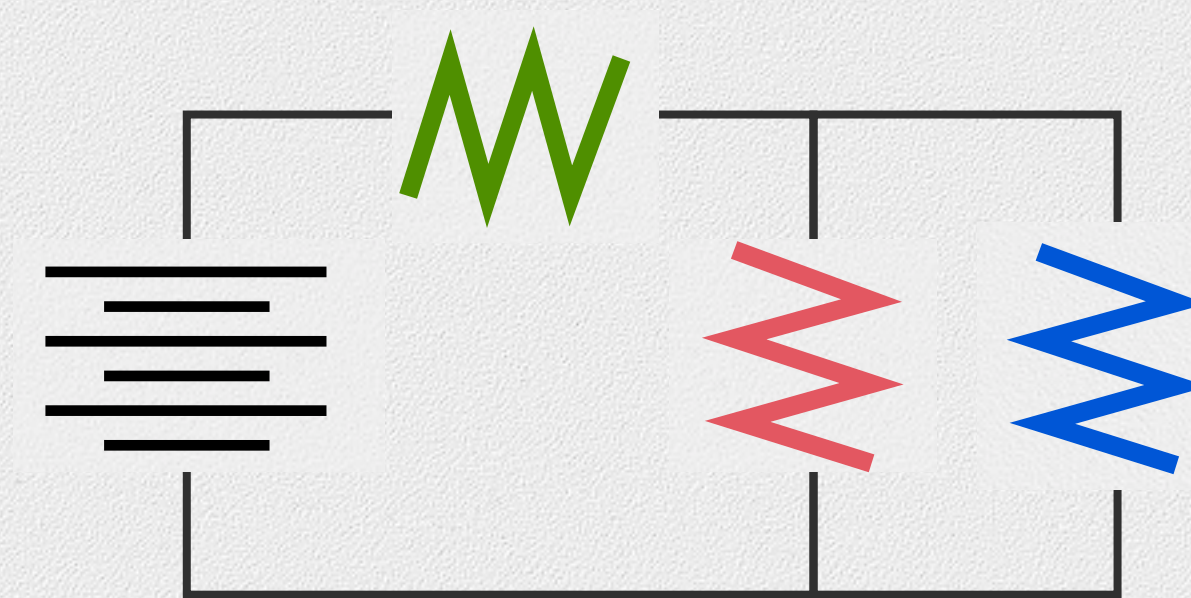

- Some in Series, some in Parallel
- Look for parts that are only one or the other
- Find an Equivalent Resistance

Combinations

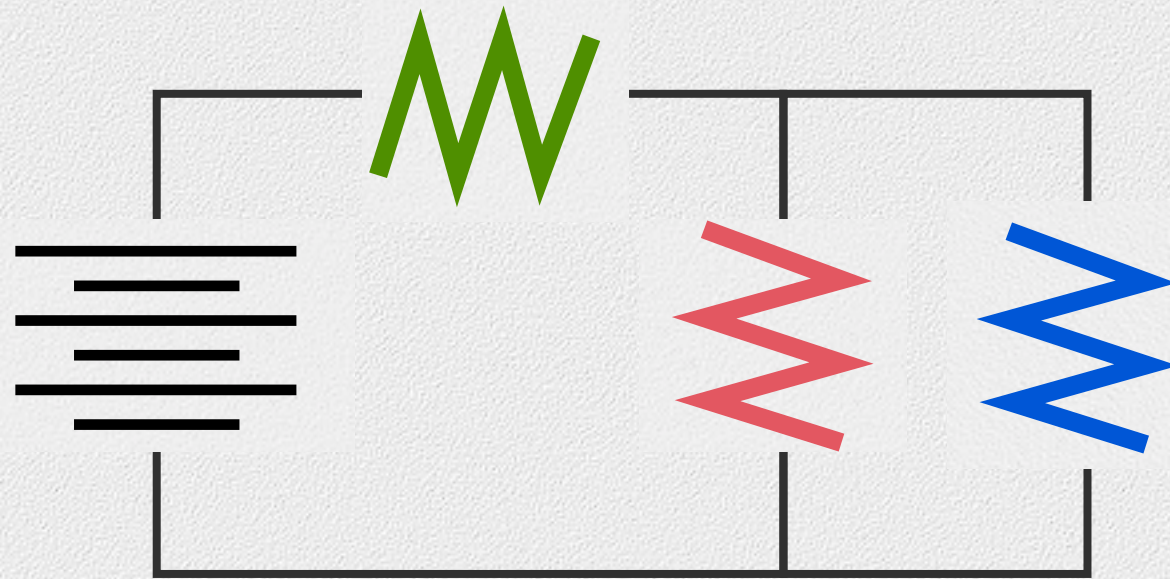

This one starts with the parallel component. Rip a piece of paper large enough to cover R_2 and R_3 .

	V (V)	I (A)	R (Ω)	P (W)
R₁			4	
R₂			18	
R₃			9	
TOTAL	60			


Combinations



A parallel combination of 18 and 9 can be replaced by a 6 ohm resistor

	V (V)	I (A)	R (Ω)	P (W)
R_1			4	
R_2			18	
R_3			9	
TOTAL	60			


Combinations

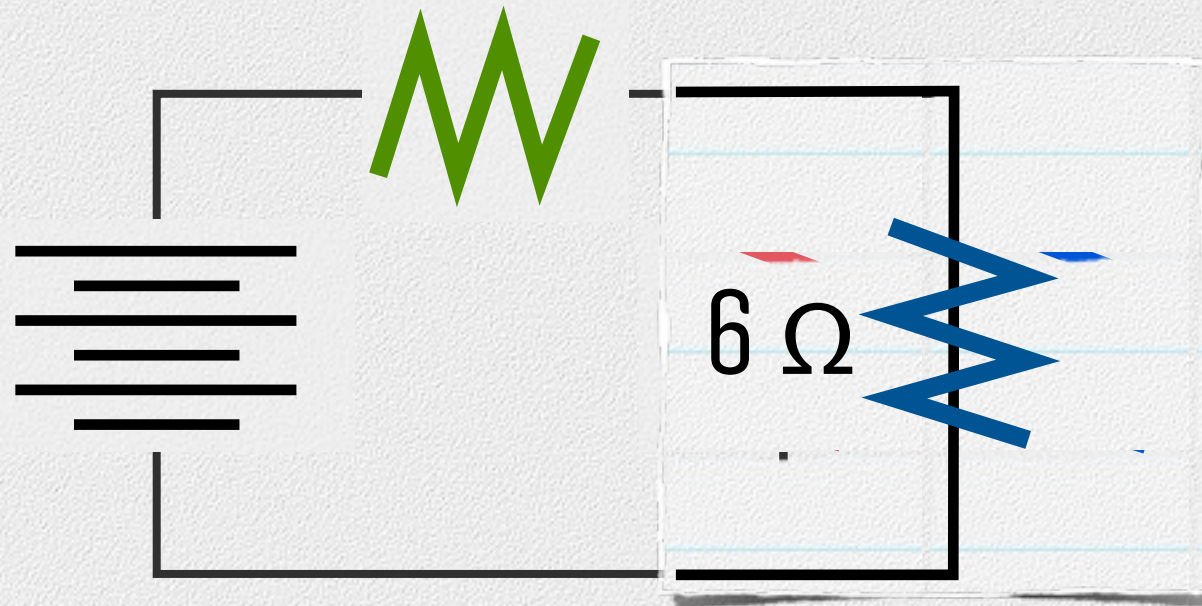

the new series of 6 and 4 creates a total resistance of 10 ohms.

	V (V)	I (A)	R (Ω)	P (W)
R_1			4	
R_2			18	
R_3			9	
TOTAL	60		10	


Combinations

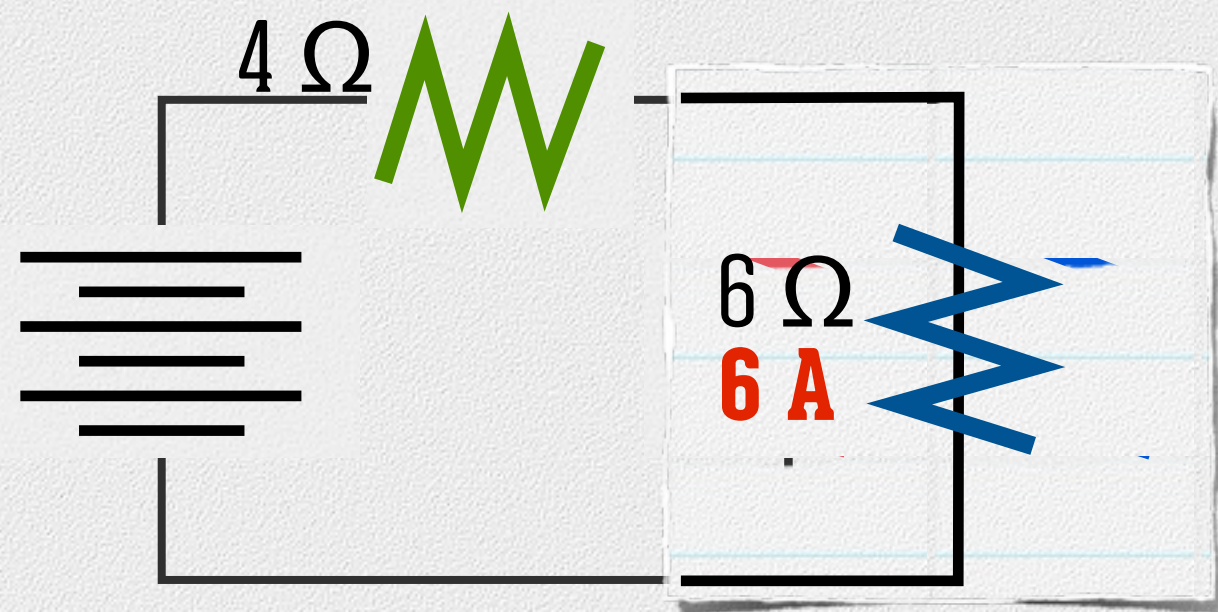

Use Ohm's Law to find a total current of 6 amperes. This is the current throughout the SERIES.

	V (V)	I (A)	R (Ω)	P (W)
R_1		6	4	
R_2			18	
R_3			9	
TOTAL	60	6	10	


Combinations

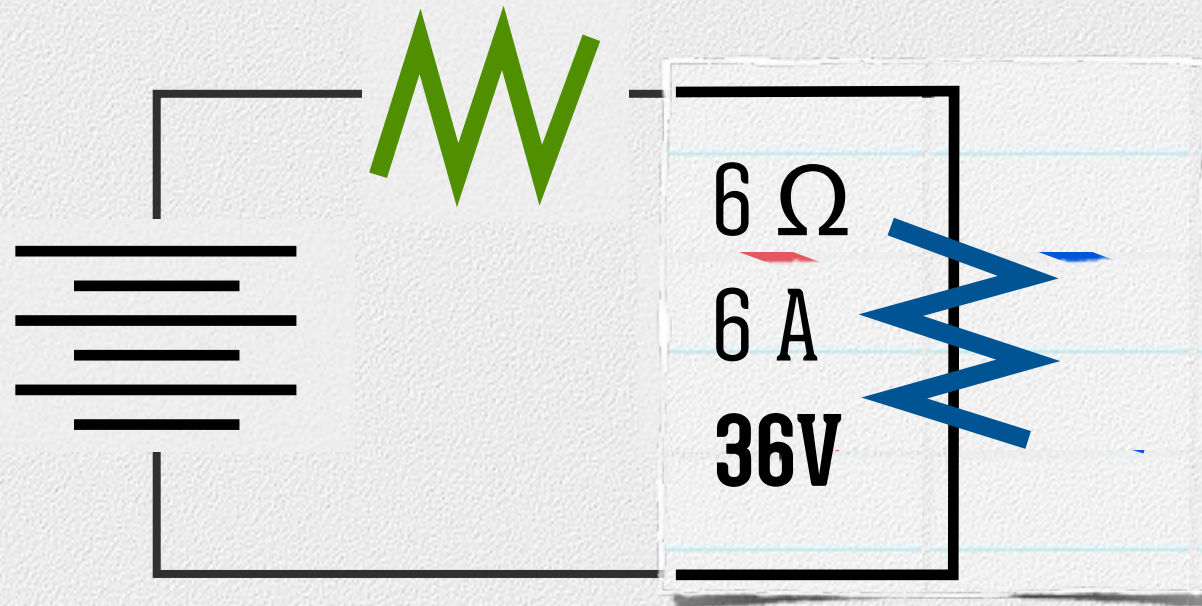

Now find the voltage for R_1 and for the paper.


	V (V)	I (A)	R (Ω)	P (W)
R_1	24	6	4	
R_2			18	
R_3			9	
TOTAL	60	6	10	

Combinations

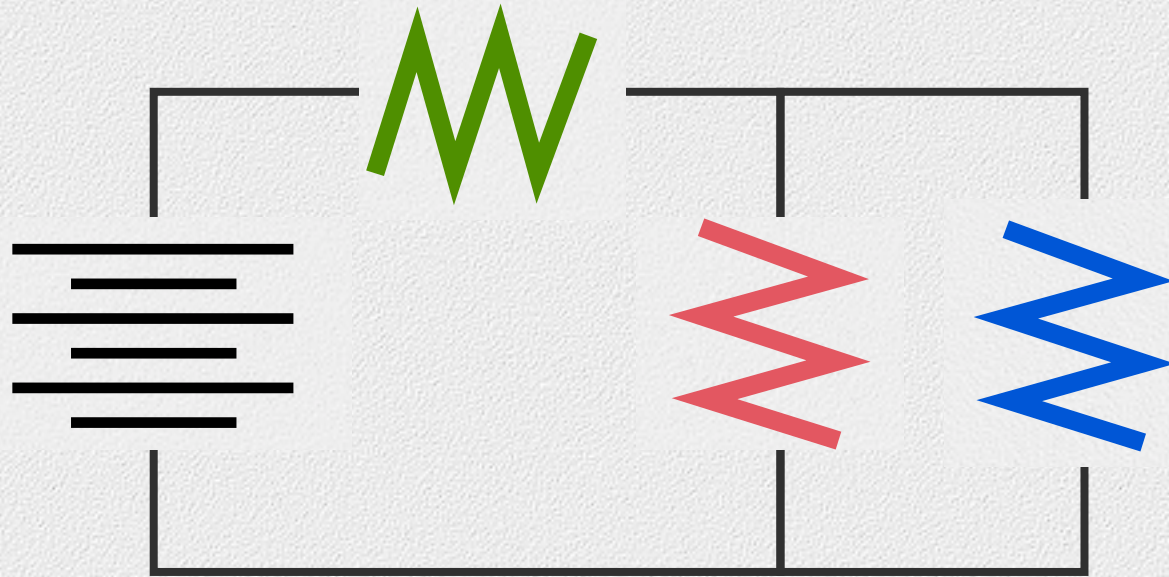


Uncover the original circuit, keep the voltage for parallel components. [if the original is a series, keep the current]

	V (V)	I (A)	R (Ω)	P (W)
R_1	24	6	4	
R_2	36		18	
R_3	36		9	
TOTAL	60	6	10	

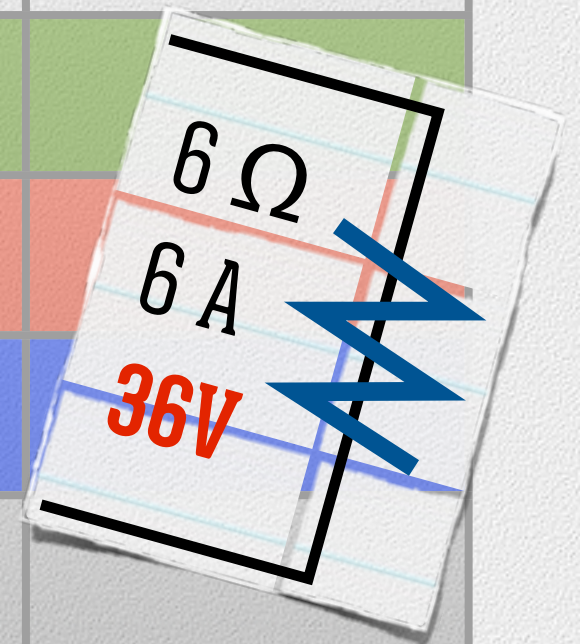


Combinations

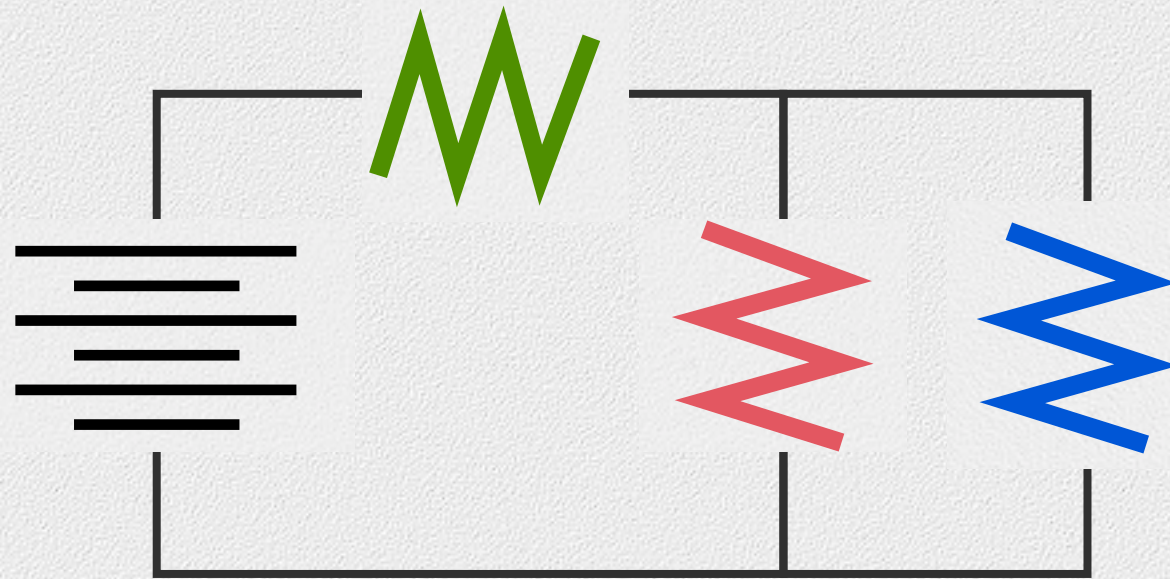

Finish the table with Ohm's Law and Power equations.


	V (V)	I (A)	R (Ω)	P (W)
R_1	24	6	4	144
R_2	36	2	18	72
R_3	36	4	9	144
TOTAL	60	6	10	360

Practice

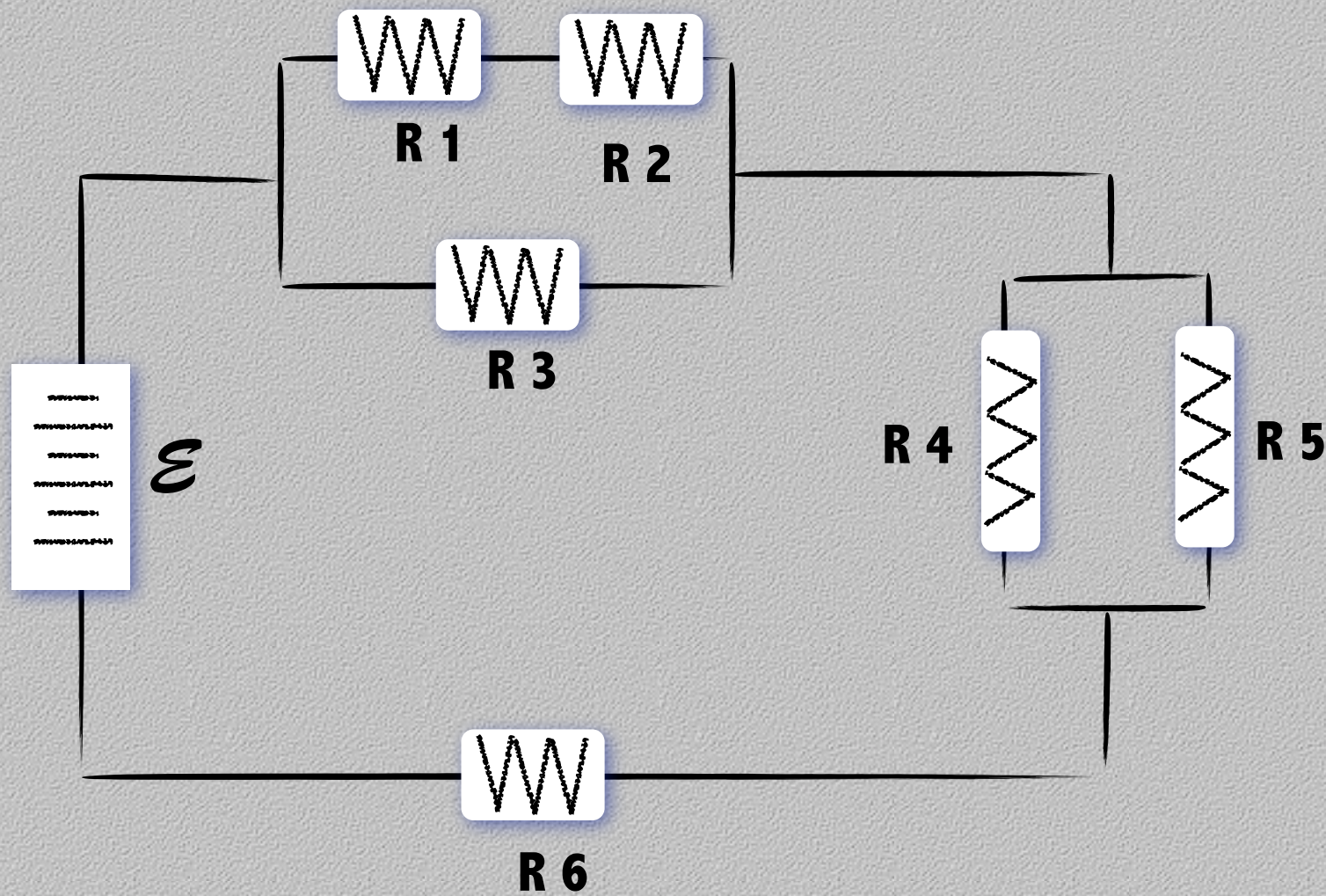


	V	I	R	P
1			10	
2			5	
3			30	
4			40	
5			10	
6			12	
T	180			

Practice

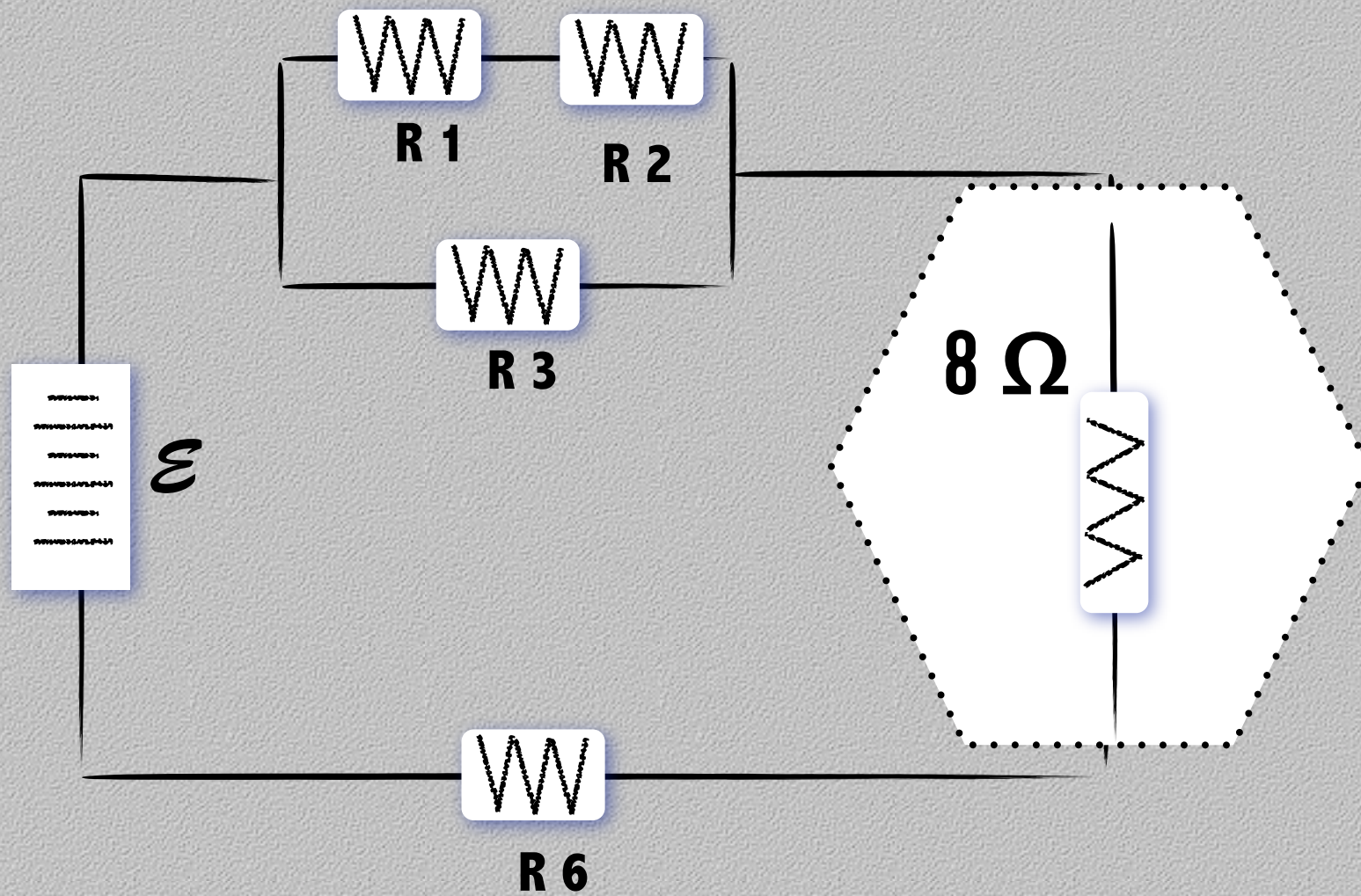


	V	I	R	P
1			10	
2			5	
3			30	
4			40	
5			10	
6			12	
T	180			

Practice

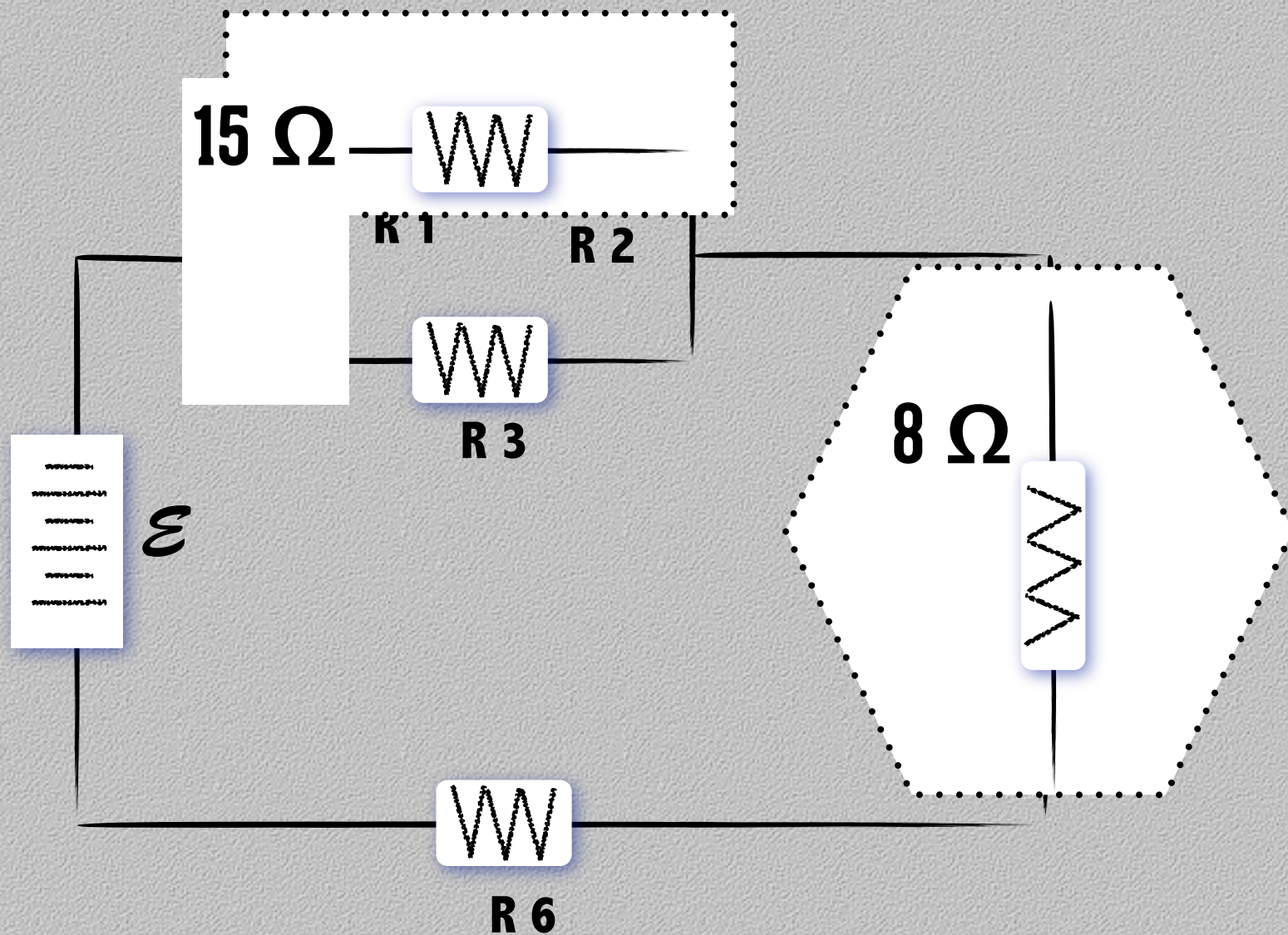


	V	I	R	P
1			10	
2			5	
3			30	
4			40	
5			10	
6			12	
T	180			

Practice

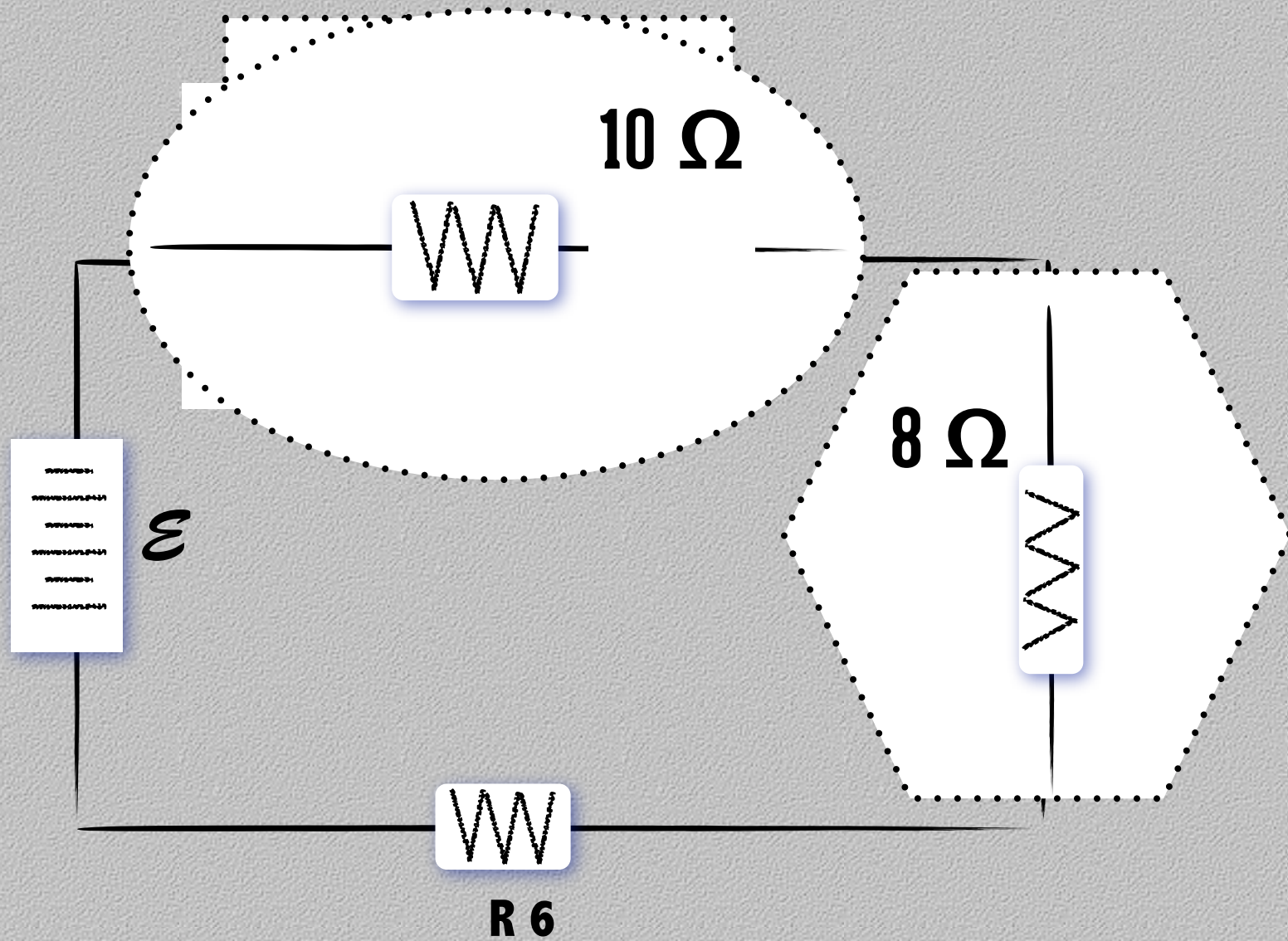


	V	I	R	P
1			10	
2			5	
3			30	
4			40	
5			10	
6			12	
T	180		30	

Practice

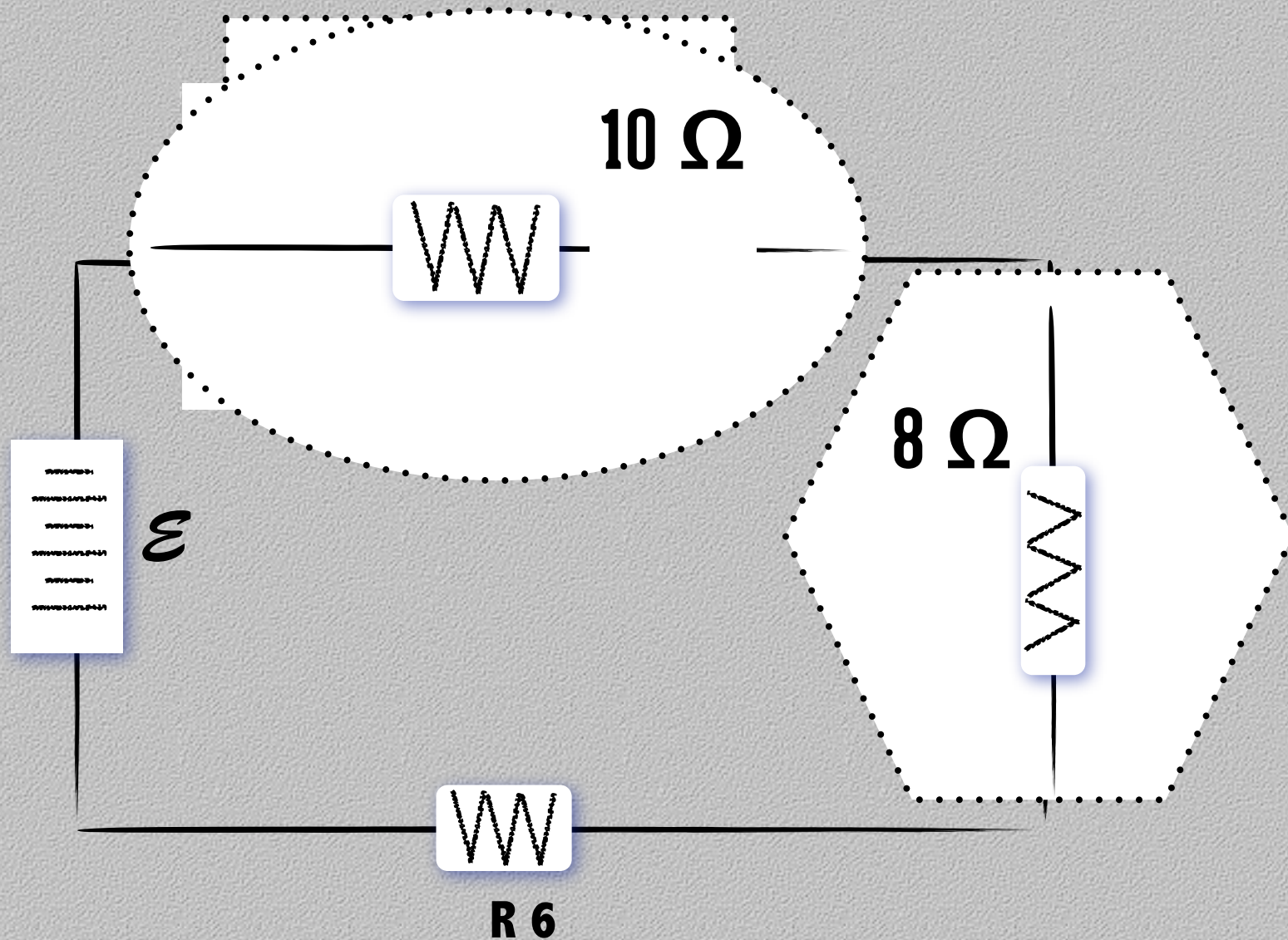


	V	I	R	P
1			10	
2			5	
3			30	
4			40	
5			10	
6			12	
T	180	6	30	

Practice

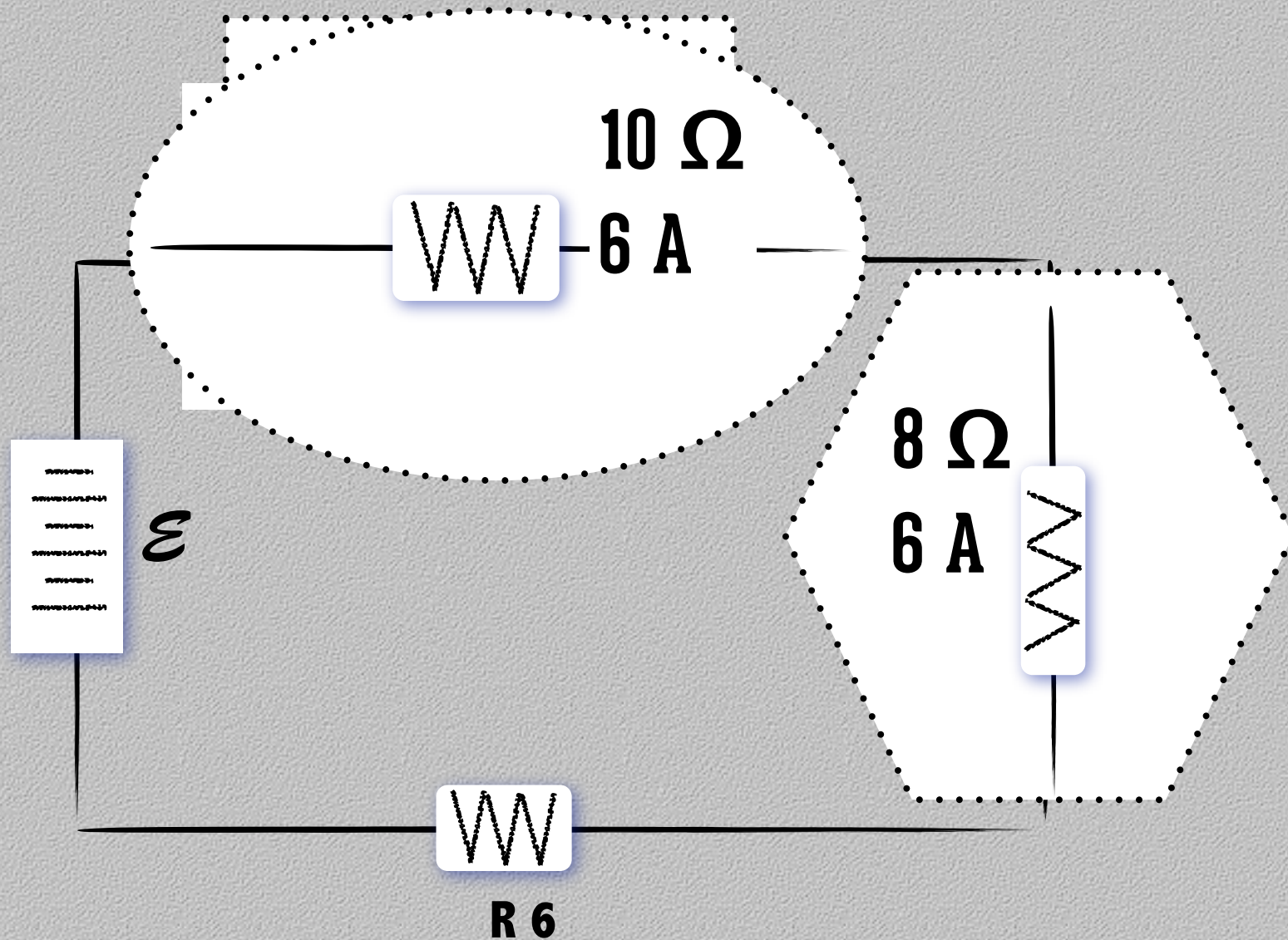


	V	I	R	P
1			10	
2			5	
3			30	
4			40	
5			10	
6		6A	12	
T	180	6	30	

Practice

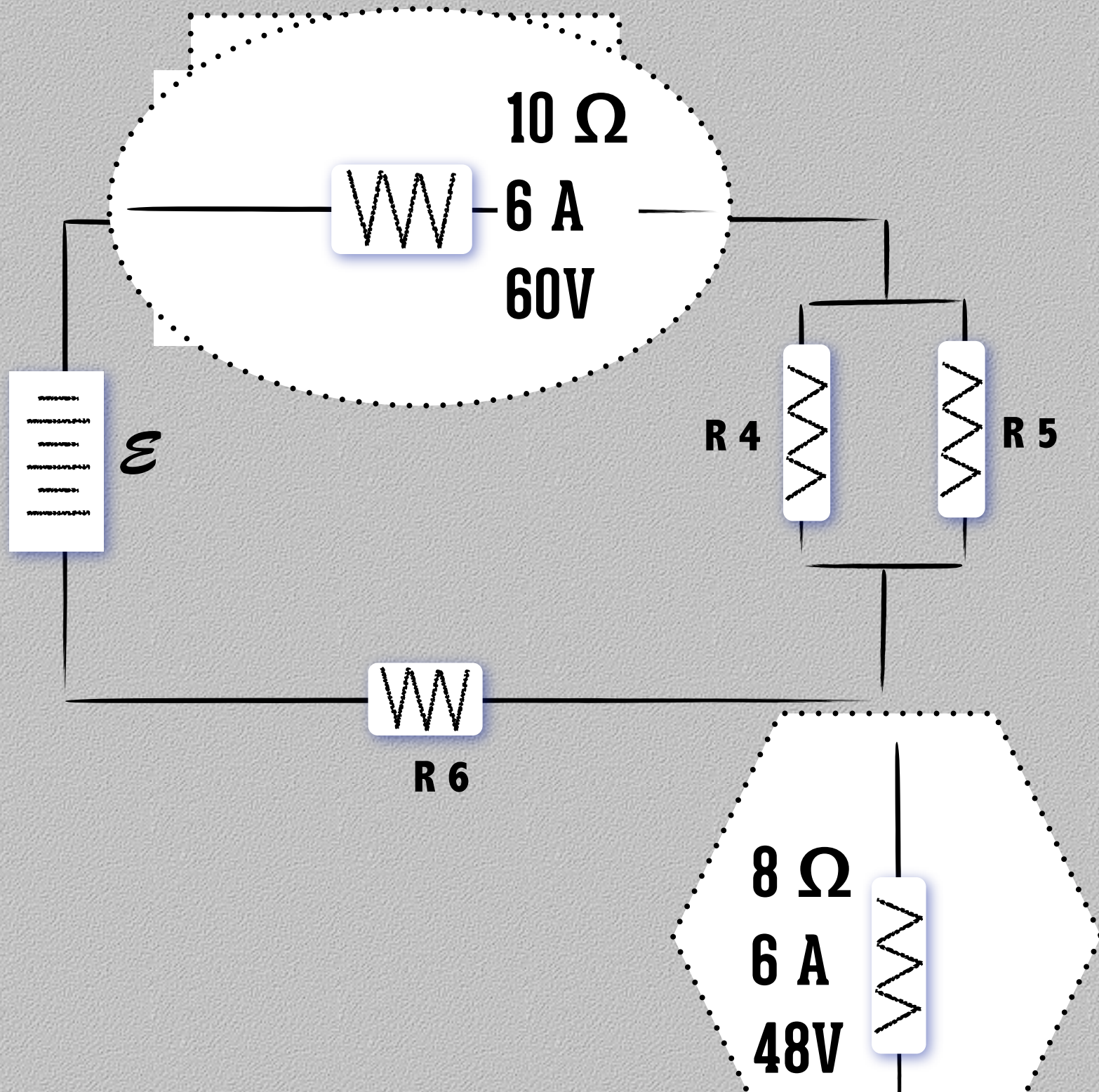


	V	I	R	P
1			10	
2			5	
3			30	
4	48V		40	
5	48V		10	
6	72V	6A	12	
T	180	6	30	

Practice

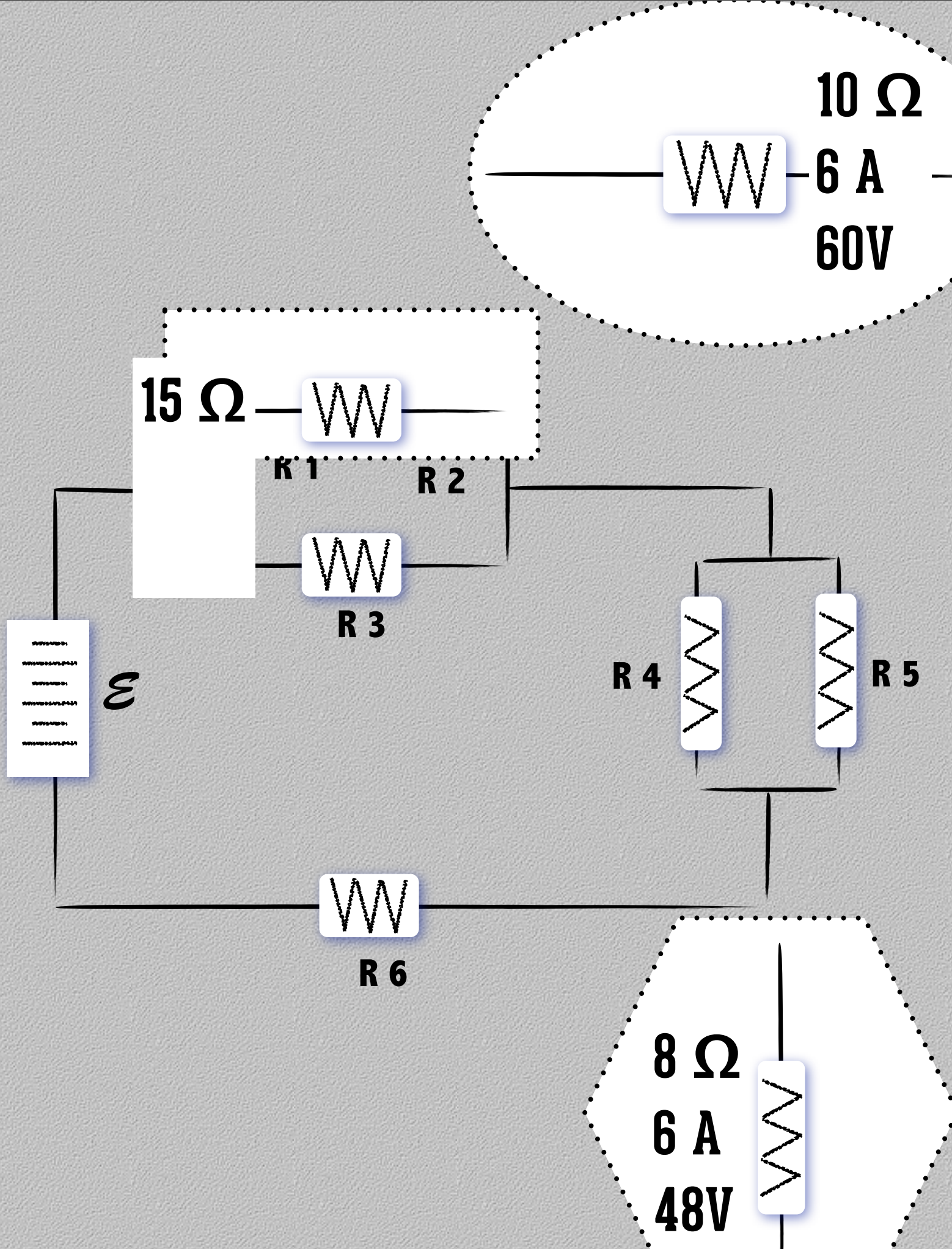

	V	I	R	P
1			10	
2			5	
3			30	
4	48V		40	
5	48V		10	
6	72V	6A	12	
T	180	6	30	

Practice

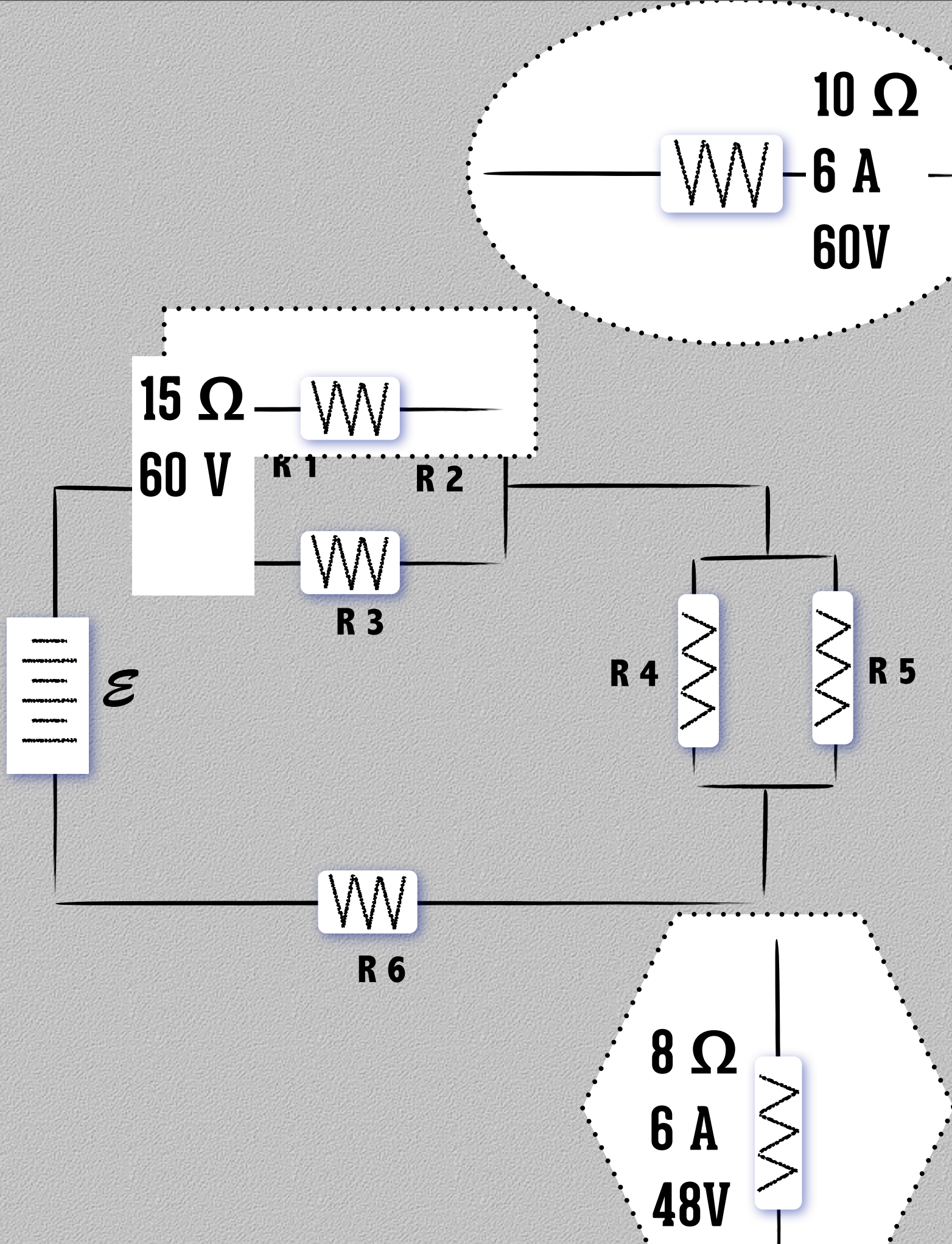


	V	I	R	P
1			10	
2			5	
3	60V		30	
4	48V		40	
5	48V		10	
6	72V	6A	12	
T	180	6	30	


15 Ω
60 V
4 A

10 Ω
6 A
60V

Practice

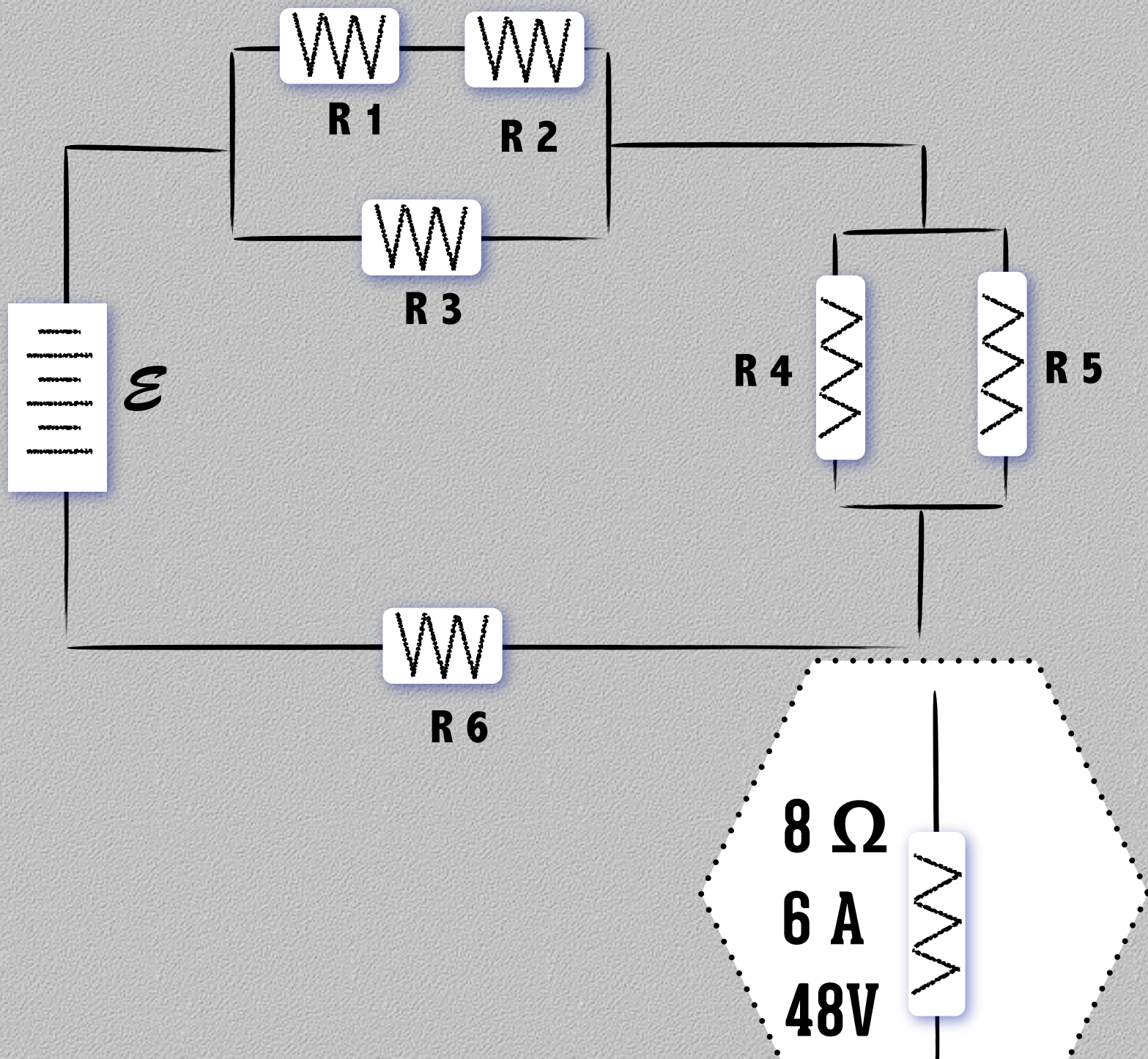

	V	I	R	P
1		4A	10	
2		4A	5	
3	60V		30	
4	48V		40	
5	48V		10	
6	72V	6A	12	
T	180	6	30	

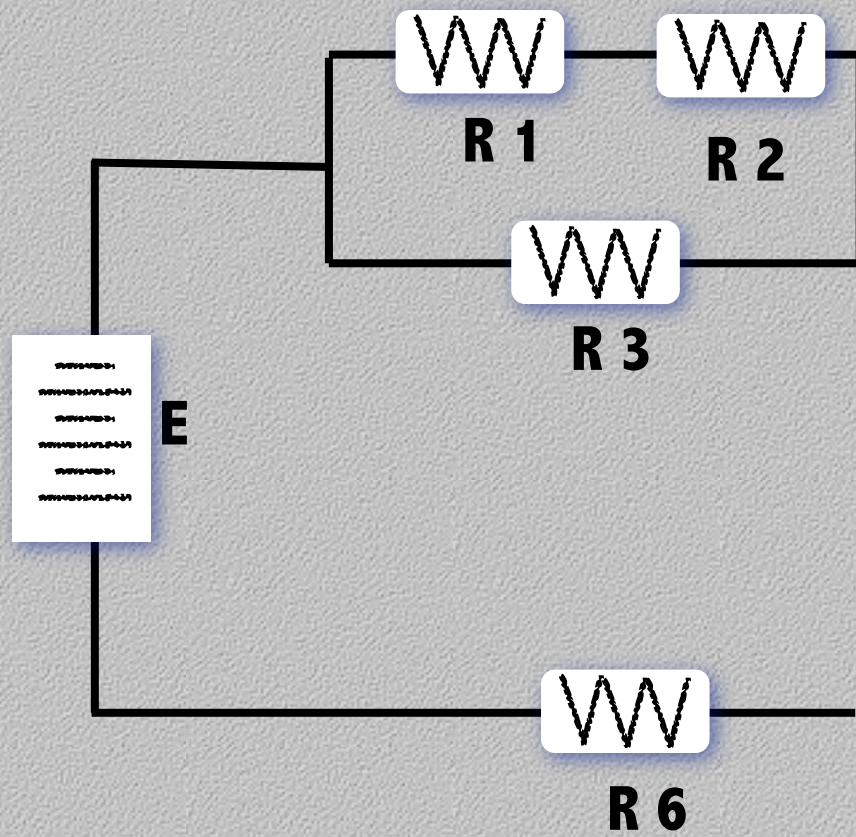


Practice

	V	I	R	P
1	40	4	10	160
2	20	4	5	80
3	60	2	30	120
4	48	1.2	40	57.6
5	48	4.8	10	230.4
6	72	6	12	432
T	180	6	30	1080

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9

Resistor Codes

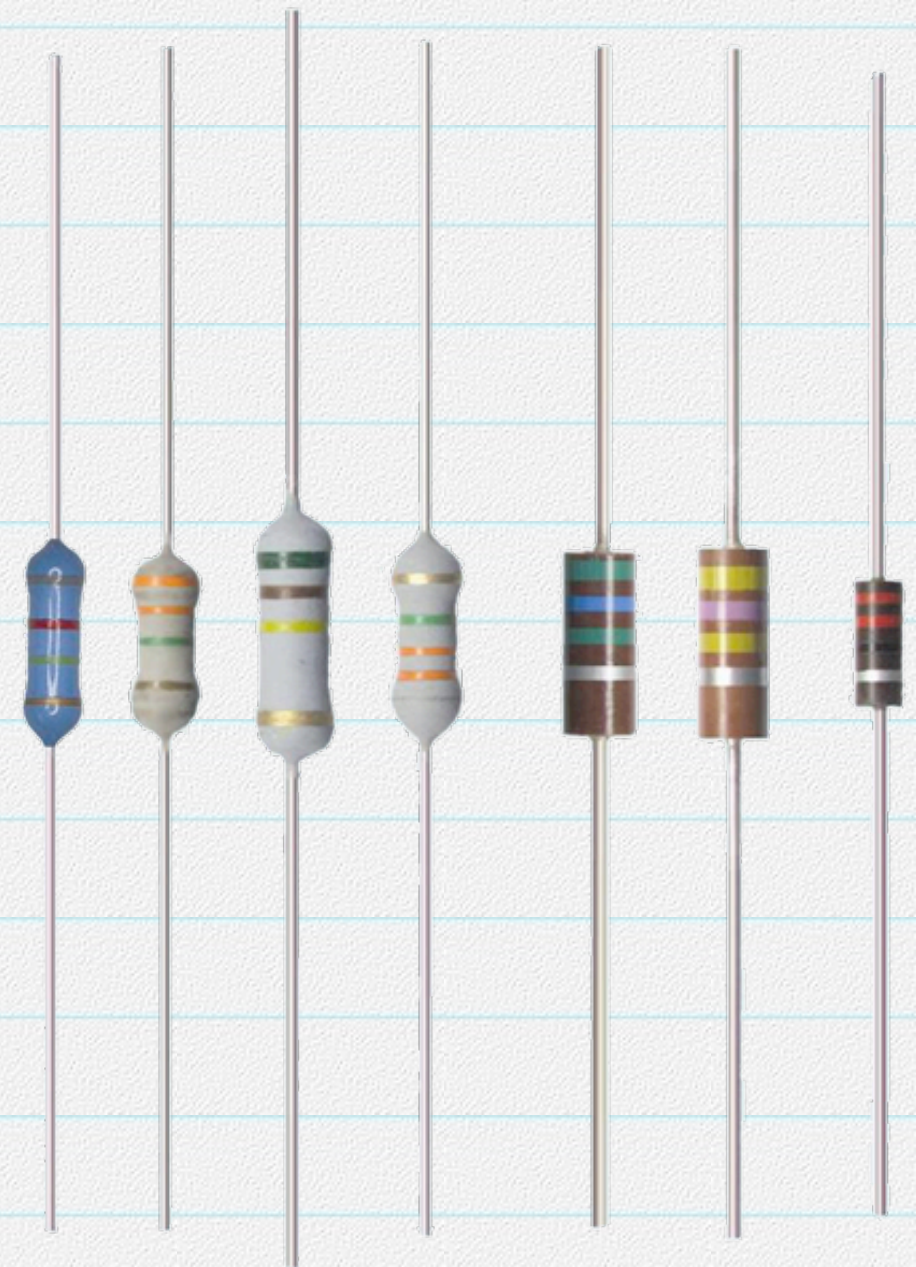

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9



Orange, Orange, Green, Gold

orange 3
orange 3
green 00,000

3,300,000 Ω \pm 5%

3.3 M Ω

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9



Gold, Yellow, Brown, Green ?



green	5	
brown	1	
yellow		0,000

510,000 Ω \pm 5%

510 k Ω

Biggest Possible Total?

102 Ω

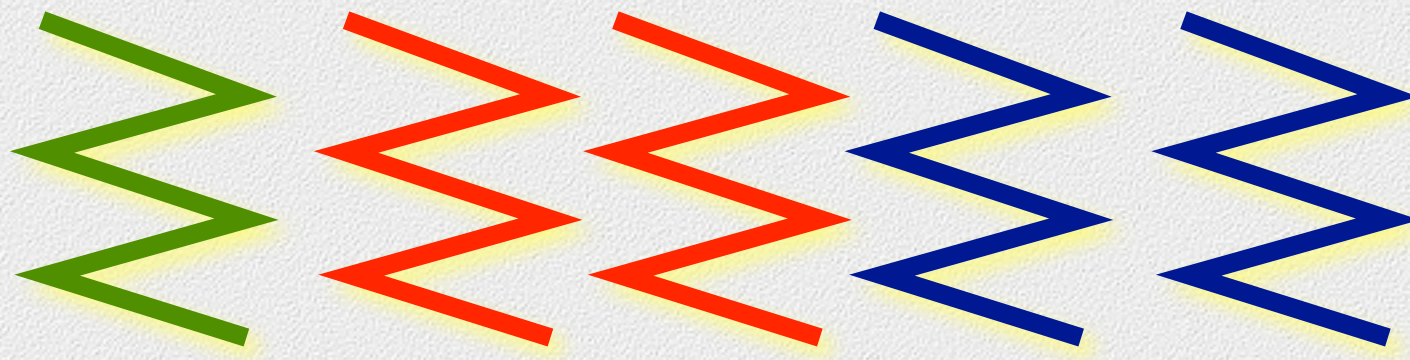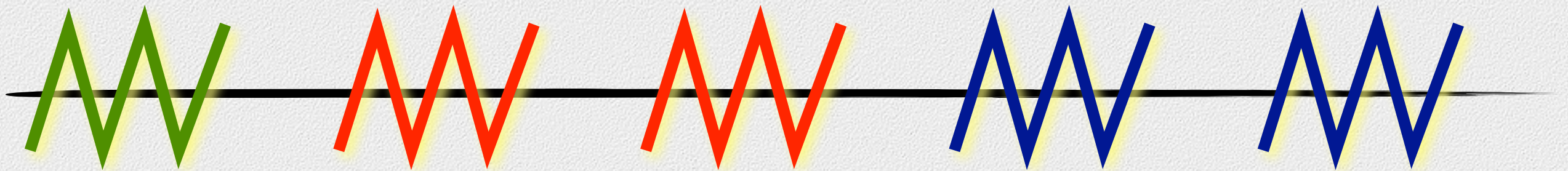

6 Ω

12 Ω



12 Ω

36 Ω

36 Ω

Smallest Possible Total?

2.57 Ω

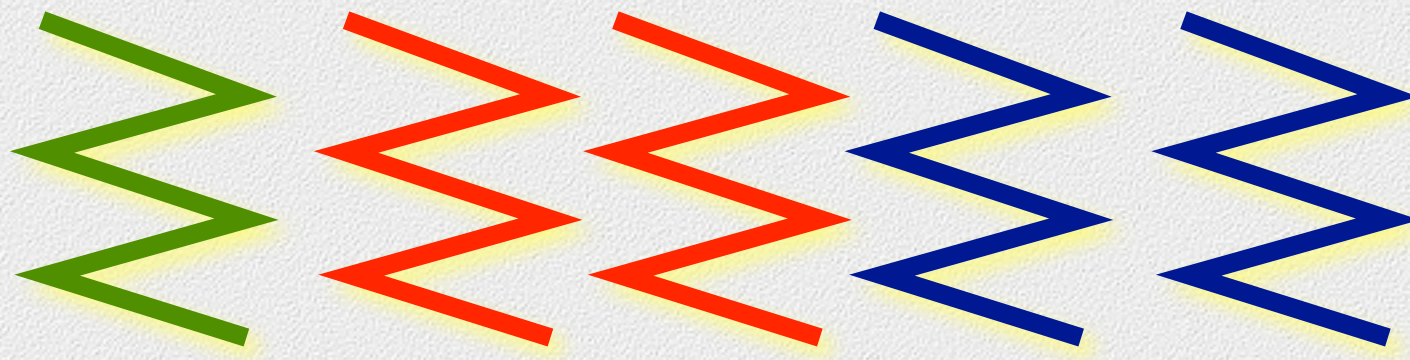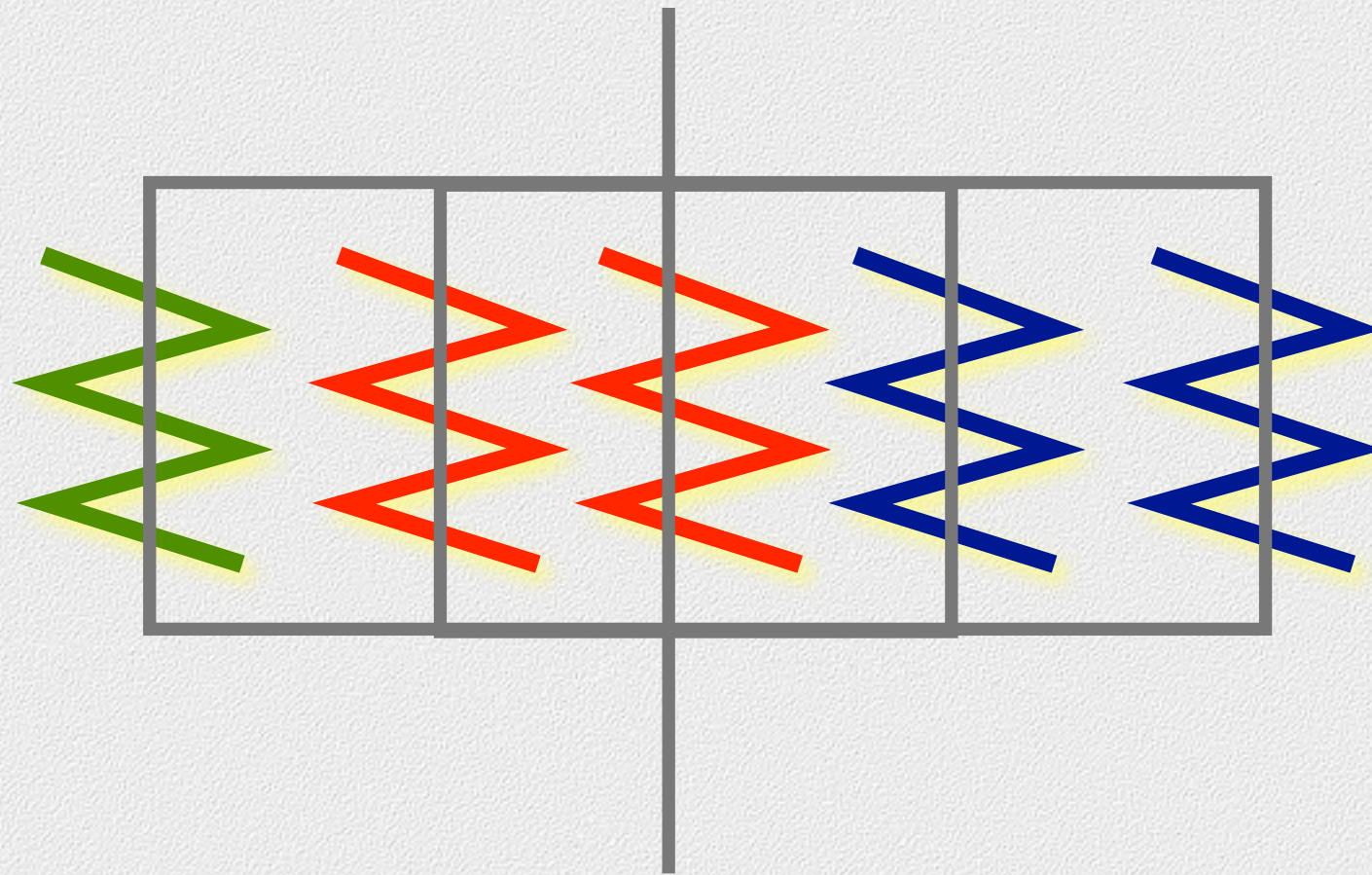

6Ω

12Ω


12Ω

36Ω

36Ω

How could you get...


$60\ \Omega$

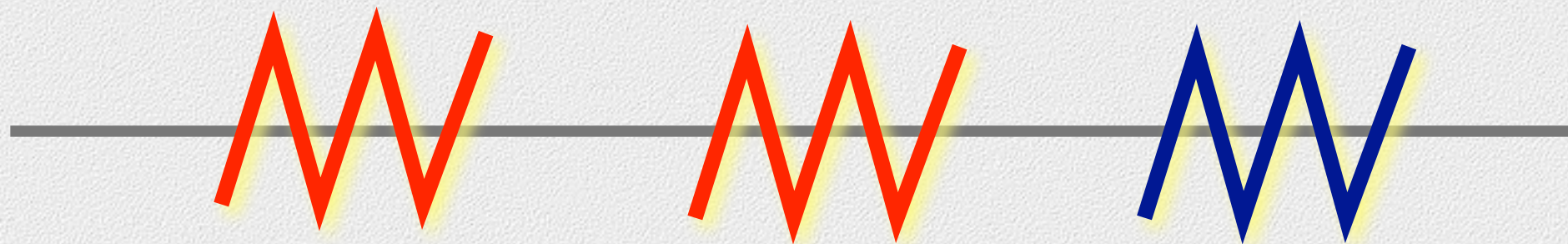


$6\ \Omega$



$12\ \Omega$

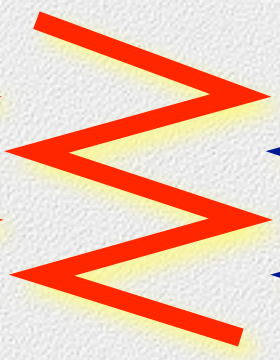

$12\ \Omega$

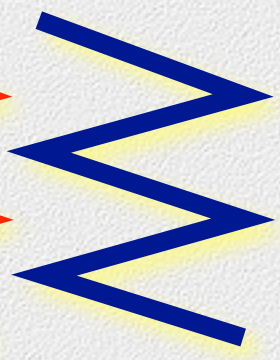


$36\ \Omega$



$36\ \Omega$

How could you get...


$4\ \Omega$

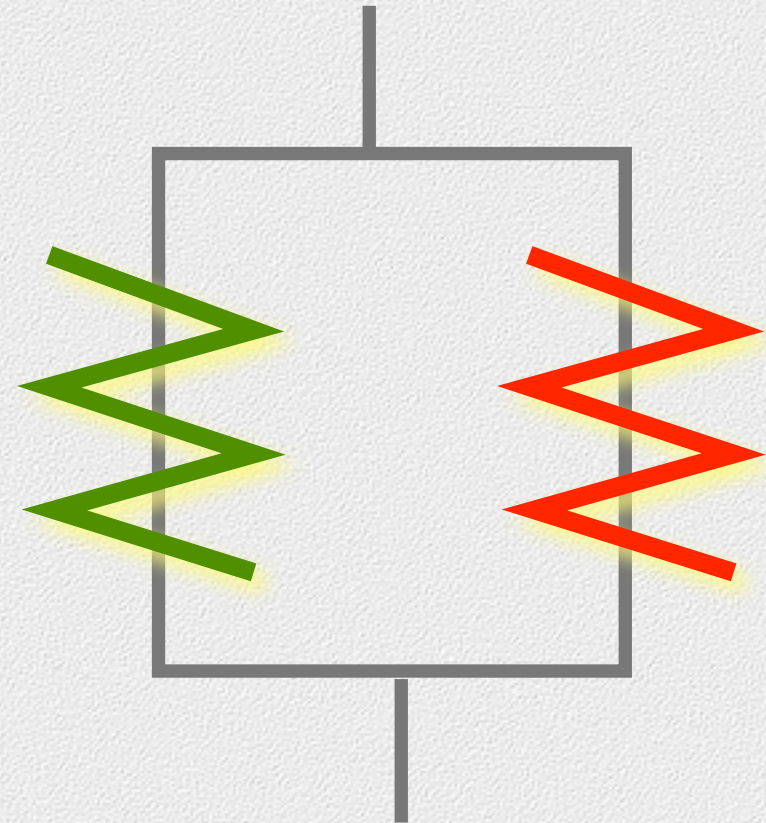


$6\ \Omega$



$12\ \Omega$

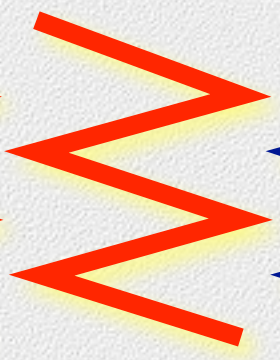

$12\ \Omega$

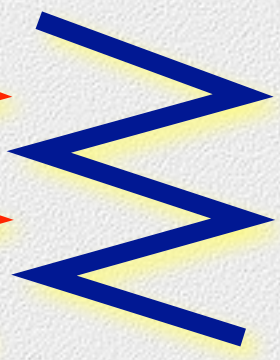

$36\ \Omega$



$36\ \Omega$

Kirchhoff's Rules

The Point Rule-

The sum of current going in to a point must equal the sum of current coming out.


$$\Sigma I_{in} = \Sigma I_{out} \qquad \Sigma I = 0$$

The Loop Rule-

A closed path that begins and ends at the same point will have no net change in potential.


$$\Sigma V = 0$$

Kirchhoff's Rules

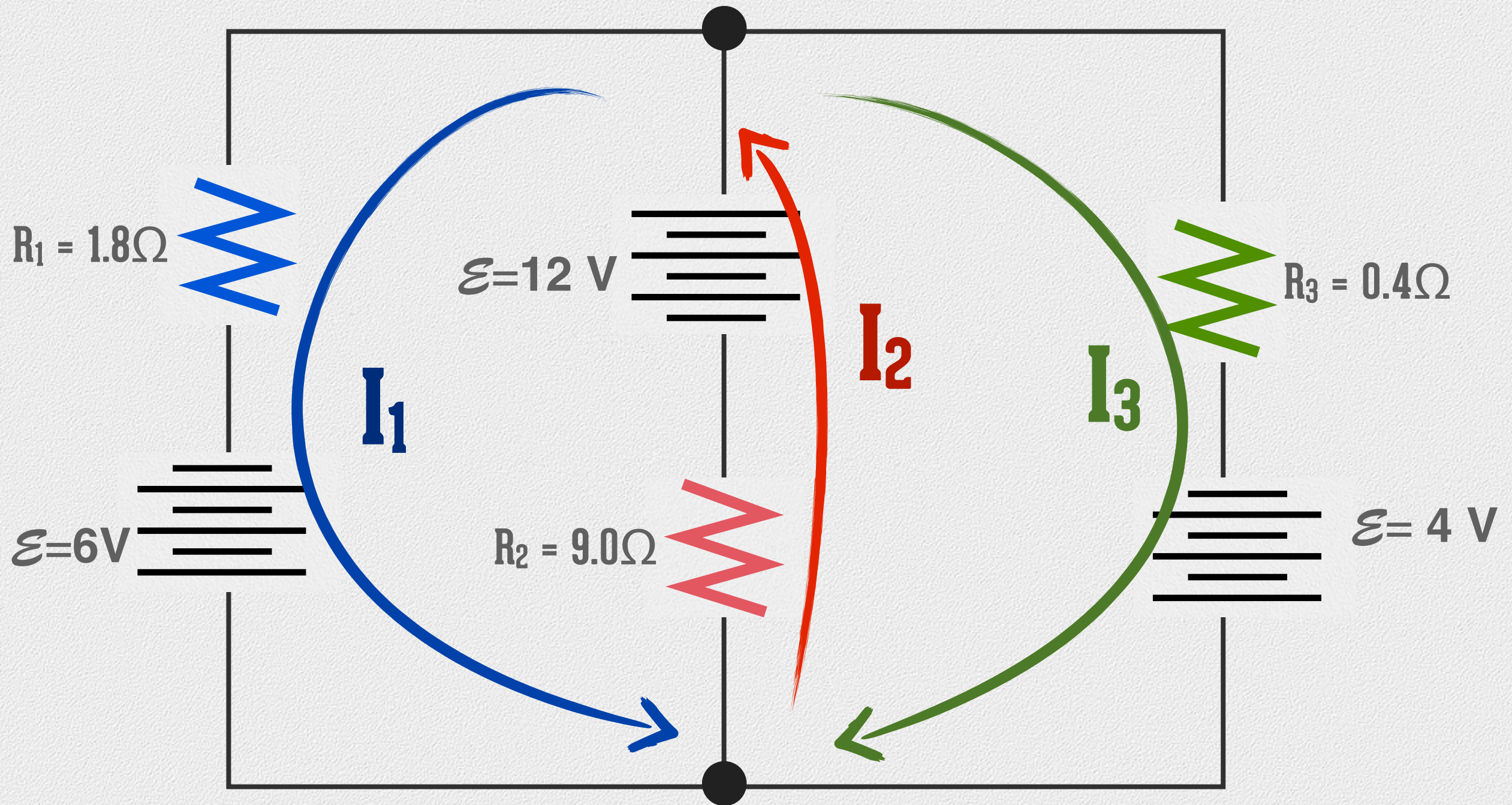

Point Rule

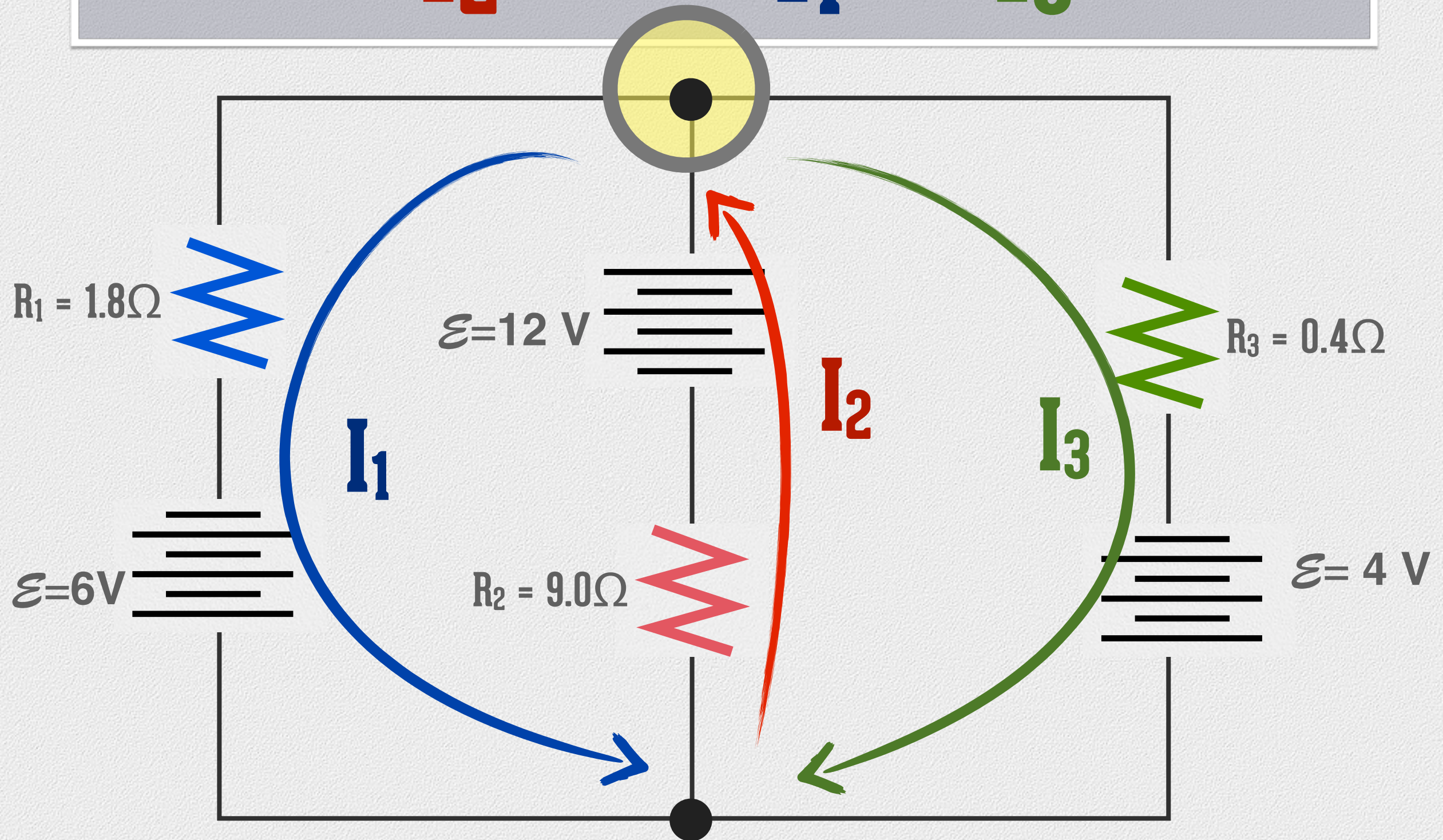
$$\Sigma I_{in} = \Sigma I_{out}$$
$$I_2 = I_1 + I_3$$



Loop Rule

$$\Sigma V = 0$$


$$-1.8I_1 + 6 - 9I_2 + 12 = 0$$

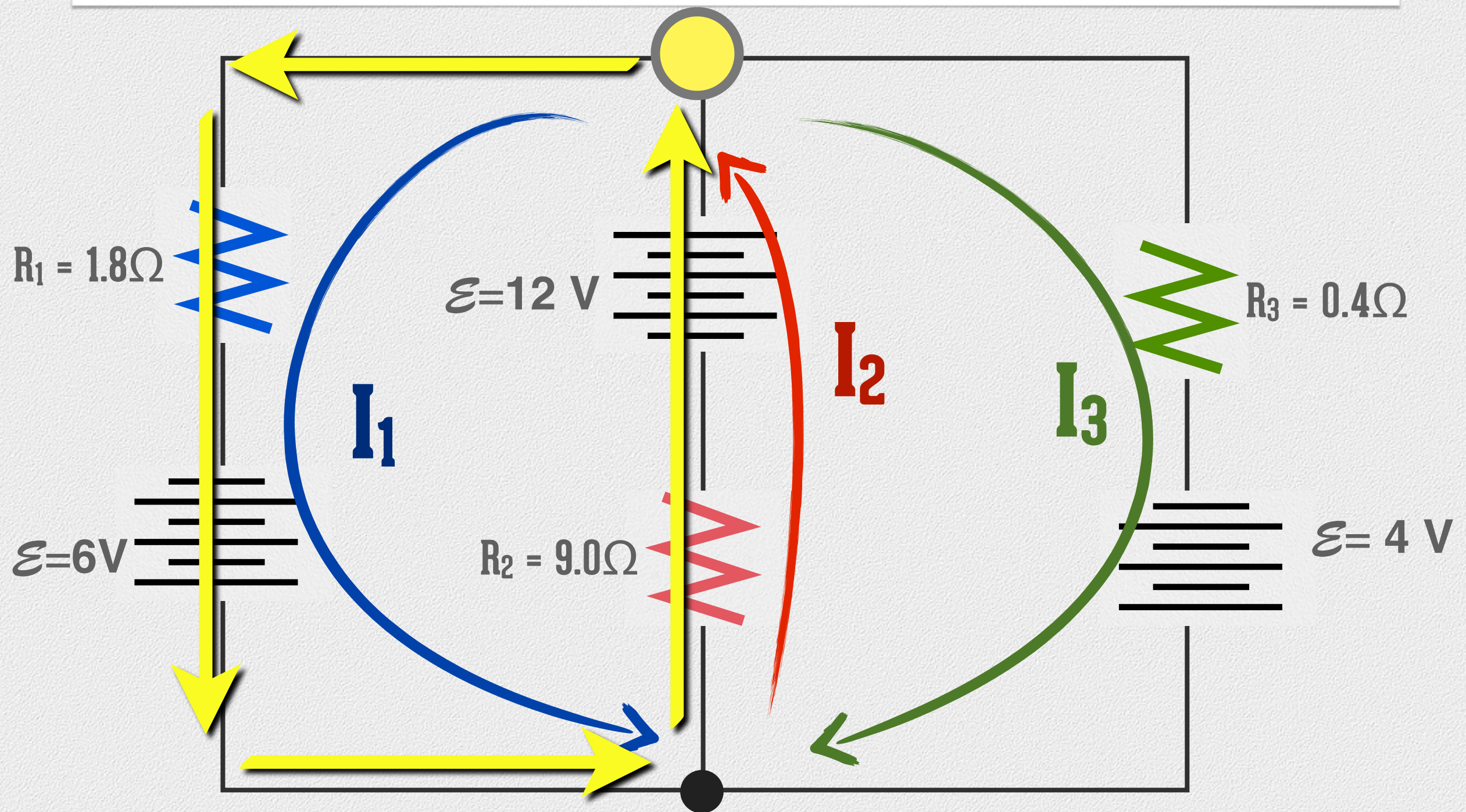

Loop Rule

$$\Sigma V = 0$$

$$-1.8I_1 + 6 - 4 + 0.4I_3 = 0$$

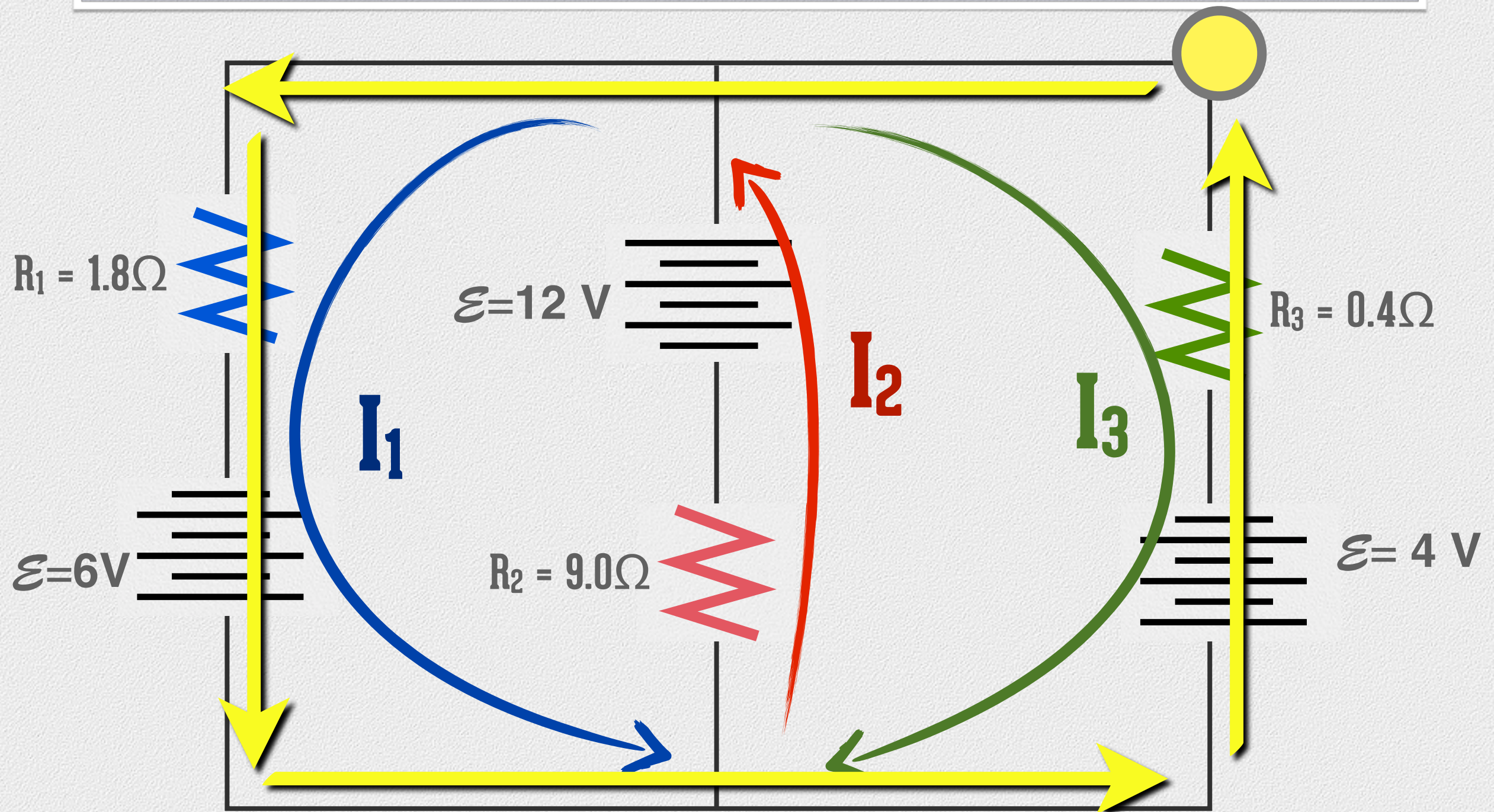

Loop Rule $-1.8I_1 + 6 - 9I_2 + 12 = 0$

Boring Algebra

simplify to: $18 - 1.8I_1 = 9I_2$

divide by 9 to get: $2 - 0.2I_1 = I_2$

$1.23 \text{ A} = I_1$

Loop Rule $-1.8I_1 + 6 - 4 + 0.4I_3 = 0$

simplify to: $2 - 1.8I_1 = -0.4I_3$

divide by -0.4 to get: $-5 + 4.5I_1 = I_3$

Point Rule $I_2 = I_1 + I_3$

substitute I_2 : $2 - 0.2I_1 = I_1 - 5 + 4.5I_1$ substitute I_3 :
 $7 = 5.7 I_1$