

THS Physics
2018-19

Electric Circuits

1

SCHMATIC

Schematic Diagrams

2

Schematic Icons

Resistor Switch Wire

Battery Cell Light Bulb

3

Ohm's Law

$$V = IR$$

$$\mathcal{E} = IR$$

Potential or Voltage (V)	in	Volts (V)
Current (I)	in	Amperes (A)
Resistance (R)	in	Ohms (Ω)

4

Electric Charge

- The charge of a single electron is 1.6021×10^{-19} Coulombs
- or... it would take 6.241×10^{18} electrons to have a Coulomb of charge
- 1 Ampere is a current of that many electrons every second.

5

Electric Power

$$P = IV$$

$$P = V^2/R$$

$$P = I^2R$$


6

Resistors in Series



The Charges have to "fight" through every resistor. This decreases the total current.

Voltage: $V_T = V_1 + V_2 + V_3$
 Current: $I_T = I_1 = I_2 = I_3$
 Resistance: $R_T = R_1 + R_2 + R_3$

7

Resistors in Series



The current starts at the top of the battery and follows a single path, clockwise, around the circuit.

	V (V)	I (A)	R (Ω)	P (W)
R ₁			2	
R ₂			4	
R ₃			6	
TOTAL	24			

8

Resistors in Series



Start with the total resistance, a simple sum of the individual values

	V (V)	I (A)	R (Ω)	P (W)
R ₁			2	
R ₂			4	
R ₃			6	
TOTAL	24		12	

9

Resistors in Series



Use the total resistance to find the total current.
 $I = V / R$
 $= 24 / 12$
 $= 2 \text{ Amperes}$

	V (V)	I (A)	R (Ω)	P (W)
R ₁			2	
R ₂			4	
R ₃			6	
TOTAL	24	2	12	

10

Resistors in Series

When you have two values for a resistor, equations will get you the other numbers.
 $V = I R$
 $V_1 = 2 \times 2 = 4 \text{ Volts}$

	V (V)	I (A)	R (Ω)	P (W)
R ₁	4	2	2	
R ₂	8	2	4	
R ₃	12	2	6	
TOTAL	24	2	12	

12

Resistors in Parallel

- The Charges have a choice of paths to follow.
- This decreases the total resistance.

Voltage: $V_T = V_1 = V_2 = V_3$
 Current: $I_T = I_1 + I_2 + I_3$
 Resistance: $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$

14

Resistors in Parallel

Add the resistors inversely.
 $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$
 $1/R_T = 1/120 + 1/60 + 1/10$
 $R_T = 8 \Omega$

	V (V)	I (A)	R (Ω)	P (W)
R ₁			120	
R ₂			60	
R ₃			10	
TOTAL	12		8 Ω	

16

Resistors in Parallel

If you are given the total Voltage (EMF), resistors in parallel all have the same Voltage.

	V (V)	I (A)	R (Ω)	P (W)
R ₁	12		120	
R ₂	12		60	
R ₃	12		10	
TOTAL	12		8 Ω	

17


Resistors in Parallel

Use Ohm's Law to find the currents
 $V = I R$
 $12 = I_1 \times 120$
 $I_1 = 0.1 \text{ Amperes}$

	V (V)	I (A)	R (Ω)	P (W)
R ₁	12	0.1	120	
R ₂	12	0.2	60	
R ₃	12	1.2	10	
TOTAL	12	1.5	8 Ω	

18

Resistors in Combination Circuits

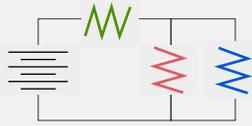


- Some in Series, some in Parallel
- Look for parts that are only one or the other
- Find an Equivalent Resistance

20

20

Resistors in Combinations

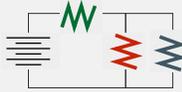


This one starts with the parallel component.
Make another resistor that will replace R_2 and R_3 .

	V (V)	I (A)	R (Ω)	P (W)
R_1			4	
R_2			18	
R_3			9	
TOTAL	60			

21

21

Resistors in Combinations

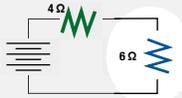


The new series of 6 and 4 creates a total resistance of 10 ohms.

	V (V)	I (A)	R (Ω)	P (W)
R_1			4	
R_2			18	
R_3			9	
TOTAL	60		10	

23

23

Resistors in Combinations

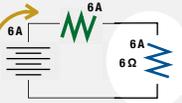


Use Ohm's Law to find a total current of 6 amperes.
This is the current throughout each series section.

	V (V)	I (A)	R (Ω)	P (W)
R_1		6	4	
R_2			18	
R_3			9	
TOTAL	60	6	10	

24

24

Resistors in Combinations

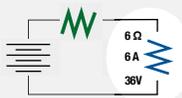

Solve for 3 values of the replacement resistor.
V, I, and R

	V (V)	I (A)	R (Ω)	P (W)
R_1		6	4	
R_2			18	
R_3			9	
TOTAL	60	6	10	

25

25

Resistors in Combinations

Uncover the original circuit, keep the voltage for parallel components.
(if the original is a series, keep the current)

	V (V)	I (A)	R (Ω)	P (W)
R ₁	24	6	4	
R ₂	36		18	
R ₃	36		9	
TOTAL	60	6	10	

26

Practice

	V	I	R	P
1		4A	10	
2		4A	5	
3	60V		30	
4	48V		40	
5	48V		10	
6	72V	6A	12	
T	180	6 A	30Ω	

28

You Have 5 Resistors

30

How could you get...

60 Ω

33

How could you get...

4 Ω

34

Resistor Codes

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9



37

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9




Green, Blue, Brown, Gold
5 6 0 (1)

560 Ω ± 5%

38

38

Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9

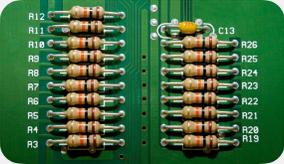

Brown, Black, Orange, Gold
1 0 000 (3)

10,000 Ω ± 5%
10 kΩ

39

39

Resistance

$$R = \frac{\rho L}{A}$$

- Resistance Ω
- resistivity Ωm
- length m
- area m²

Material	Resistivity ρ (Ω·m)	Material	Resistivity ρ (Ω·m)
Aluminum	2.82 × 10 ⁻⁸	Carbon	3.5 × 10 ⁻⁵
Copper	1.72 × 10 ⁻⁸	Carbonium	6.0 ⁶
Gold	2.44 × 10 ⁻⁸	Silicon	20-2300 ⁶
Iron	9.7 × 10 ⁻⁸	Insulators	
Mercury	95.8 × 10 ⁻⁸	Mica	10 ¹¹ -10 ¹⁷
Nickel (alloy)	60.0 × 10 ⁻⁸	Rubber (sheet)	10 ¹³ -10 ¹⁴
Silver	1.59 × 10 ⁻⁸	Teflon	10 ¹⁰
Stainless	7.0 × 10 ⁻⁸	Wood (parallel)	3 × 10 ¹¹

The values pertain to temperatures near 20 °C.
*Manufactured by Vishay



40

40
